

# MODULE-3

14/02/2020

Non-linear ckt      Signal processing ckt

Amp linear ckt = -ve feedback

Non-linear ckt = +ve feedback

Op-amp as NON-linear Circuits:-

- 1) +ve feedback
- 2) i/p voltage { differential i/p }
- 3)  $+V_{sat} \rightarrow +V_{CC} - 1$   
 $-V_{sat} \rightarrow -V_{EE} + 1$  } op switches between  $+V_{sat}$  &  $-V_{sat}$

$$M = \frac{V_o}{V_i}$$

$$V_{i(diff)min} = \frac{\pm V_{CC}}{M_{min}} = \frac{\pm 15V}{5000} = \underline{\underline{300\mu V}}$$


$V_{i(diff)max}$  { depends on supply } =  $2 \times V_{CC}$

- 1) Comparator
- 2) Schmitt Trigger
- 3) Astable Multivibrator
- 4) Mono stable Multivibrator

\* Comparator:

- ① Non-inverting zero crossing detector { ZCD }
- ② Inverting ZCD.
- ③ Voltage level detector
- ④ Capacitor coupled crossing detector

1) Non-inverting ZCD:

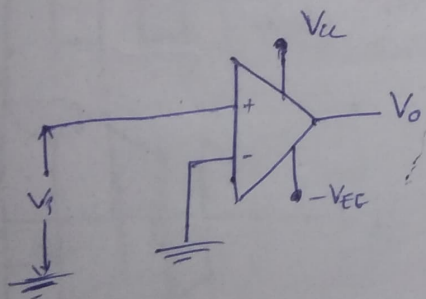


if  $V_i > 0$  &  $V_i < 0$


$V_i > 0$        $+V_{sat} = V_o$  { non-inv > inv }

$V_i < 0$        $-V_{sat} = V_o$  { inv > non-inv }

Waveform:

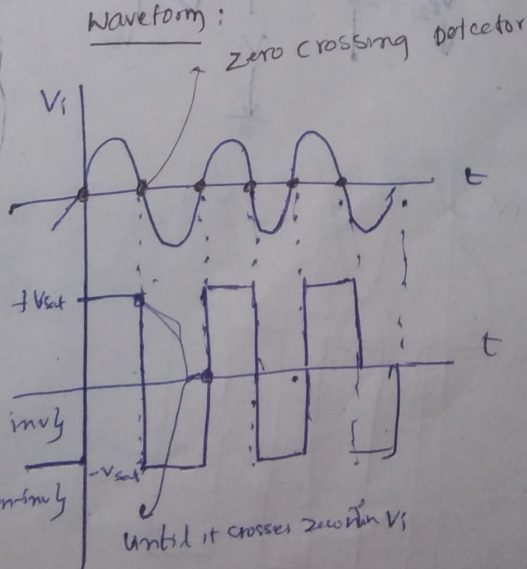


Inverting ZCD:

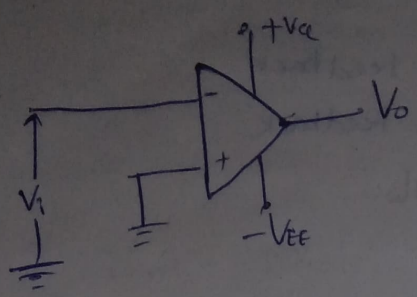

if  $V_i > 0$   
 $V_o = -V_{sat}$   
 if  $V_i < 0$   
 $V_o = +V_{sat}$

WAVE FORMS:

• zero <sup>crossing</sup> detecting

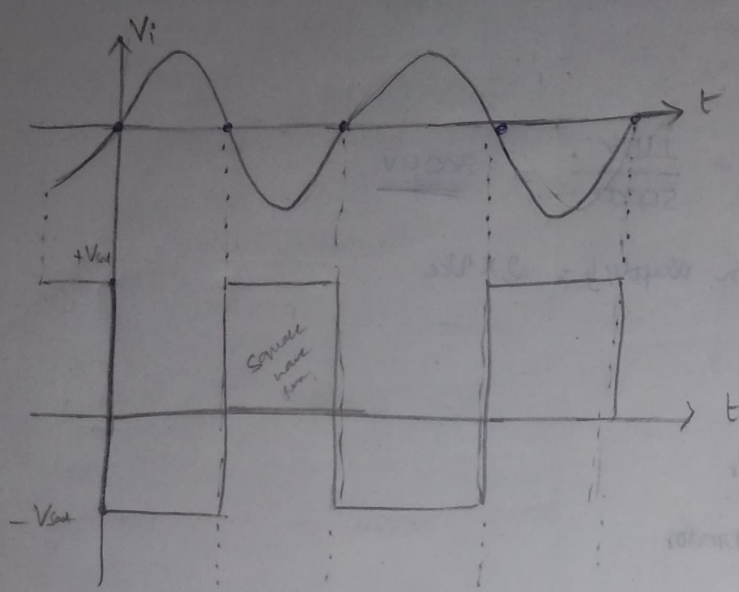


- 1) Diagram
- 2) condition example
- 3) waveform


3) VOLTAGE LEVEL DETECTOR:

1)  $V_i > V_{R2}$   
 $V_o = -V_{sat}$


2)  $V_i < V_{R2}$   
 $V_o = +V_{sat}$

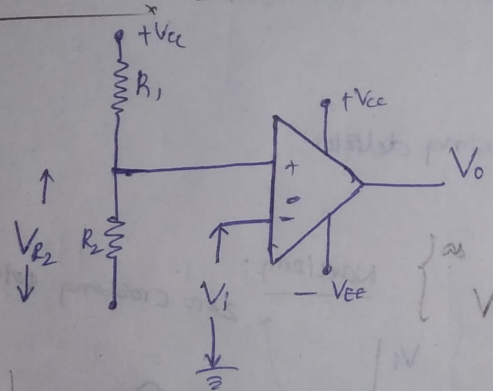

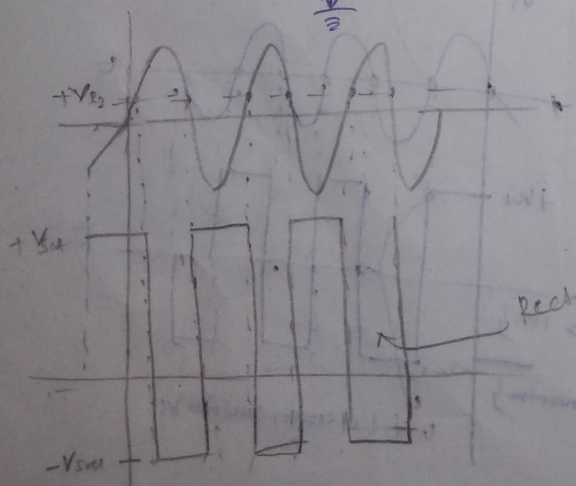as connected to +Vcc,  $V_{R2}$  is the voltage  
 $V_{R2} = \frac{V_{cc}}{1+R_1/R_2}$



Rectangular wave form

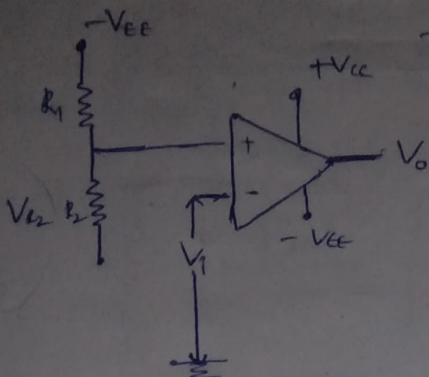

$$1) V_i > V_{R2}$$

$$V_o = -V_{sat}$$


$$2) V_i < V_{R2}$$

$$V_o = +V_{sat}$$

$V_i$  { Applied to inverting terminal


$$V_{R2} = \left( \frac{-V_{CC}}{R_1 + R_2} \right) (R_2)$$

$V_{R2} = -V_C$  Reference voltage

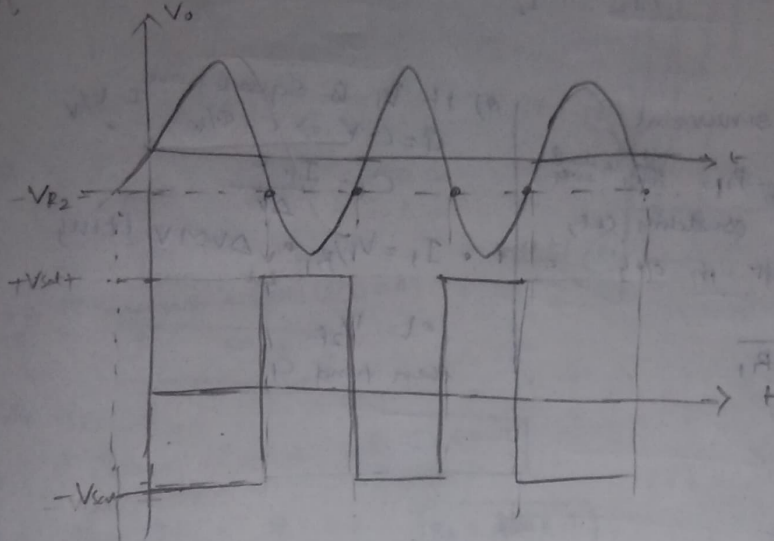

18/Feb/20
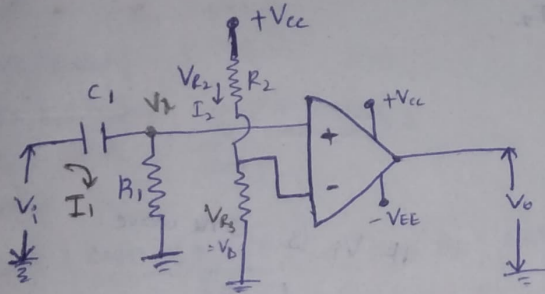
#### 4) Capacitor Coupled crossing detector:




$$V_i < V_B, V_o = -V_{sat}$$

$$V_i > V_B, V_o = +V_{sat}$$

$$+V_{sat} = +V_{CC} - 1V$$

$$-V_{sat} = -V_{EE} + 1V$$

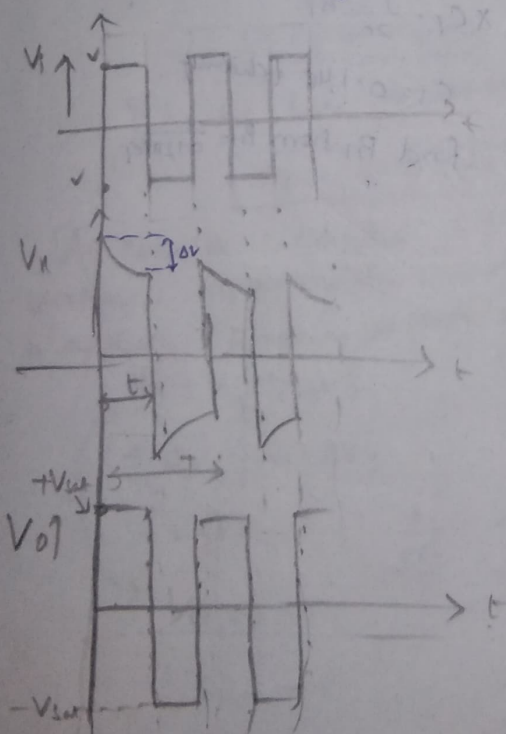immediate change capacitor act as short ckt.



$$T = 2t$$

$$t = T/2$$

$$t = 1/2f$$

$$T = 1/f$$

# DESIGN {741}

- 1)  $B_1 = \frac{0.1 V_{BE}}{I_{B \text{ Max}}}$
- 2) Let  $I_2 = 100 I_{B \text{ Max}}$
- 3) Assume  $V_{R_3} = V_B = 0.1V$
- 4)  $R_3 = \frac{V_{R_3}}{I_2} = \frac{V_B}{I_2}$
- 5)  $R_2 = \frac{V_{CC} - V_{R_3}}{I_2} = \frac{V_{CC} - V_B}{I_2} = \frac{V_{R_2}}{I_2}$

6) To find  $C_1$

1) if  $V_i$  is sinusoidal

$$X_{C_1} = \frac{1}{20} R_1 \quad \frac{1}{2\pi f C_1} = \frac{1}{20} R_1$$

{ Since it is buffering ckt, to avoid phase shift in op/amp }

$$C_1 = \frac{1}{2\pi f R_1}$$

2) if  $V_i$  is square wave  
 $Q = C \cdot V \Rightarrow C = Q/V = I \cdot t / V$   
 $C_1 = \frac{I_1 \cdot t}{\Delta V}$   
 $I_1 = V_B / R_1 \quad \Delta V = 1V \text{ (typical)}$

$t = 1/2f$   
 then find  $C_1$

## BIFET:

1) Let  $R_2 = 1M\Omega$

$$R_2 = \frac{V_{R_2}}{I_2} \quad \frac{V_{R_2}}{I_2} = \frac{V_{CC} - V_B}{I_2}$$

$$I_2 = \frac{V_{CC} - V_B}{R_2}$$

$$2) R_3 = \frac{V_B}{I_2} = \frac{V_{R_3}}{I_2}$$

3) to find  $C_1$

if  $V_i$  is square wave

$$\frac{V_i}{R_1} = I_1 \quad \text{Choose } C_1 = 0.1 \mu F$$

find  $I_1$  from  $\left\{ C_1 = \frac{I_1 \cdot t}{\Delta V} \right\}$

where  $\Delta V = 1V \quad t = 1/2f$

\* find  $R_1$

$$R_1 = \frac{V_i}{I_1}$$



if  $V_i$  is sine wave

$$X_{C_1} = \frac{1}{20} R_1$$

$C_1 = 0.1 \mu F$  (choose)

find  $R_1$  from  $R_1 = \frac{1}{0.12\pi f C_1}$

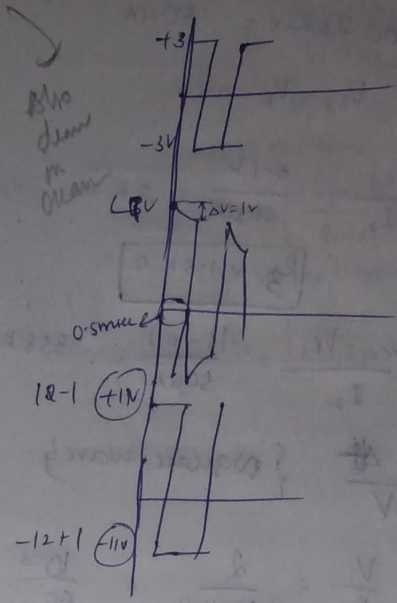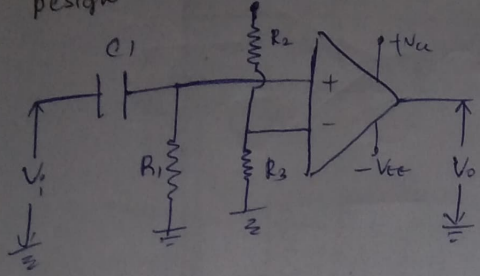A Capacitor Coupled crossing detector is to handle 1 kHz square wave i/p with peak-peak 6V design a suitable ckt Using 741 op-amp with  $\pm 12V$  supply.



$f = 1 \text{ KHz}$   
 $t = \frac{1}{2f} = 0.5 \text{ msec}$   
 $V_{sat} = \pm 11V$

1)  $R_1 = \frac{0.1 V_{BE}}{I_{Bmax}} = \frac{(0.1)(0.7)}{500\mu A} = 140K\Omega$

$R_1 = 180K\Omega$

2)  $I_2 = 100 I_{Bmax} = (100)(500\mu A)$

$I_2 = 50\mu A$

3)  $V_{R3} = V_B = 0.1V$

4)  $R_3 = \frac{0.1}{500\mu A} = 2K\Omega$

$R_3 = 1.8K\Omega$

5)  $R_2 = \frac{V_{cc} - V_{R3}}{I_2} = \frac{12 - 0.1}{500\mu A}$

$R_2 = 23.8K\Omega$

6) Square wave  $\{ V_i \}$

$t = 0.5 \text{ msec}$   
 $I_1 = \frac{V_i}{R_1} = \frac{3V}{120K\Omega} = 25\mu A$

$\Delta V = 1V$

$C_1 = \frac{(25\mu A)(0.5 \text{ msec})}{1} = 12.5 \text{ nF} = 0.0125 \mu F$

if  $C_1$  is higher " $\Delta V$ " get effected & " $t$ " also get change so,  $C_1$  take approx value of " $C_1$ "

$C_1 = 0.012 \mu F$

A capacitor coupled crossing detector is to provide an o/p voltage approximately  $\pm 1V$  when a 3KHz with  $\pm 2V$  square wave is applied. Design a suitable detector using bipolar op-amp  $\rightarrow 741$

$\pm 1.7V \{ V_{sat} \}$

$\pm 2V \{ V_i = 2V \}$

$f = 3KHz$

$\frac{1}{2f} = \frac{1}{6KHz} = 0.1667 \text{ msec}$

$V_{cc} = \pm 18V$

$$1) R_1 = \frac{0.1 V_{BE}}{I_{Bmax}} = 140 K\Omega$$

$$R_1 \approx 120 K\Omega$$

$$2) I_2 = 100 I_{Bmax} = 50 \mu A$$

$$3) \text{ Assume } V_{E3} = V_B = 0.1 V$$

$$4) R_3 = \frac{V_{E3}}{I_2} = \frac{0.1 V}{50 \mu A} = 2 K\Omega$$

$$R_3 \approx 1.8 K\Omega$$

$$5) R_2 = \frac{V_{CC} - V_{E3}}{I_2} = \frac{18 - 0.1}{50 \mu A} = 358 K\Omega$$

$$R_2 = 330 K\Omega$$

$$6) C_1 = \frac{I_1 \Delta t}{\Delta V} \quad \left\{ \begin{array}{l} \text{square wave} \\ \text{wave} \end{array} \right.$$

$$I_1 = \frac{V_i}{R_1} = \frac{2}{120 K\Omega} = \frac{10^{-3}}{60}$$


$$C_1 = \frac{\left(\frac{10^{-3}}{60}\right) \left(\frac{10^{-3}}{6}\right)}{(1)} = \frac{10^{-6}}{360} = 2777 \text{ PF}$$

$$C_1 = 2700 \text{ PF}$$


ST/26/20


Inverting Schmitt trigger (or) Regenerative comparator (or) sine to square wave converter.

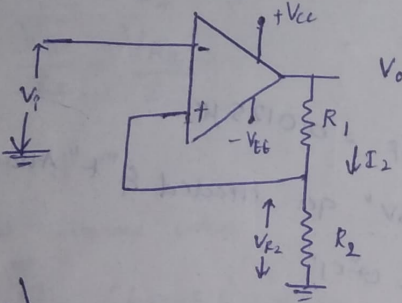- Uses +V<sub>e</sub> feedback
- Symmetrical


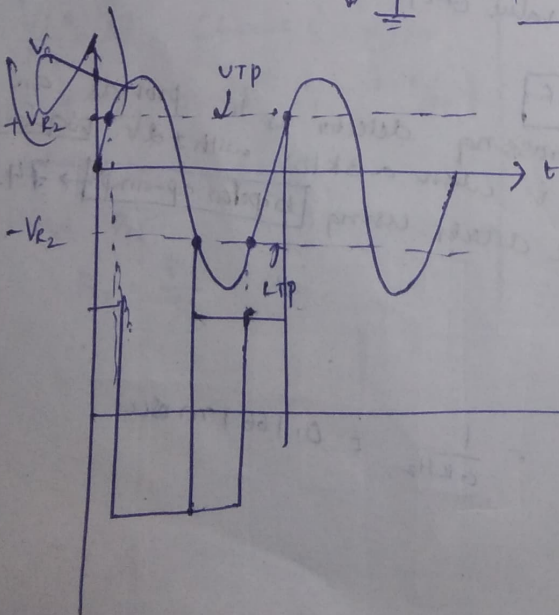
$$\begin{aligned} +V_{sat} &= V_{CC} - 1V \\ -V_{sat} &= -V_{CC} + 1V \end{aligned}$$



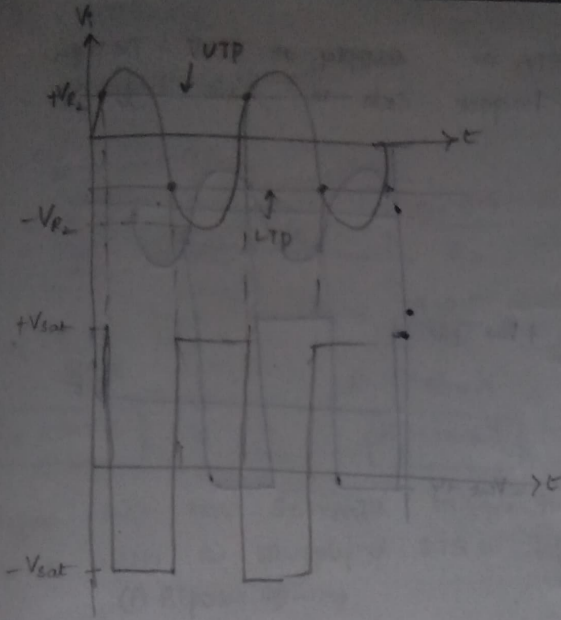

$$V_{E2} = \left( \frac{V_o}{R_1 + R_2} \right) R_2$$

$$\text{If } V_i < V_{E2}$$

$$V_o = +V_{sat}$$

$$\text{If } V_i > V_{E2}$$

$$V_o = -V_{sat}$$


UTP } upper triggering points

$$V_{R2} = \left( + \frac{V_{sat}}{R_1 + R_2} \right) R_2 \rightarrow \text{UTP}$$

LTP } lower triggering points

$$V_{R2} = \left( - \frac{V_{sat}}{R_1 + R_2} \right) R_2 \rightarrow \text{LTP}$$

### I/O Characteristics

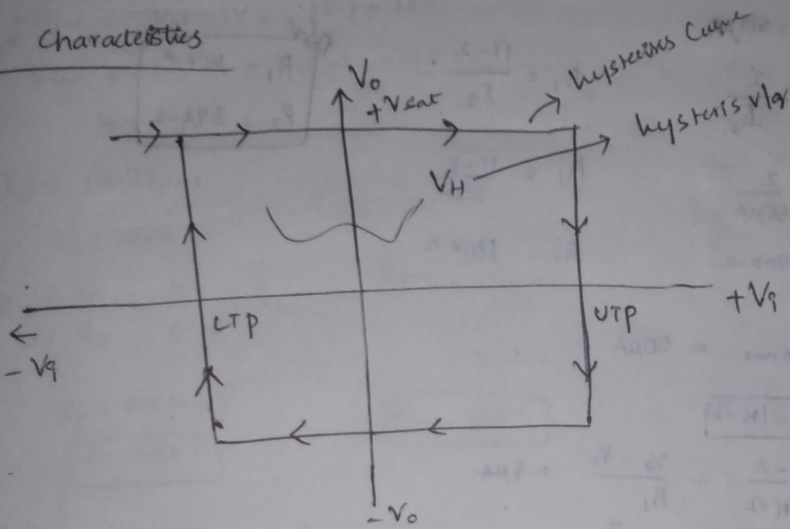

$$V_H = \text{UTP} - \text{LTP}$$

$$= \left[ \left( + \frac{V_{sat}}{R_1 + R_2} \right) R_2 \right] - \left[ - \frac{V_{sat}}{R_1 + R_2} \times R_2 \right]$$

Design { 741 }

$$\text{Let } I_2 = 100 I_{B \text{ Max}}$$

$$R_2 = \frac{\text{Triggering Voltage}}{I_2}$$

$$R_1 = \frac{V_o - \text{Triggering Voltage}}{I_2}$$

{ BIFET / LF553 }

$$\text{Choose } R_1 = 1 \text{ M}\Omega$$

find  $I_2$ .



find  $R_2$

$$R_2 = \frac{\text{Triggering Voltage}}{I_2}$$

Numericals

① Using 741 op-amp with an inverting Schmitt trigger points  $\pm 0.2V$ .

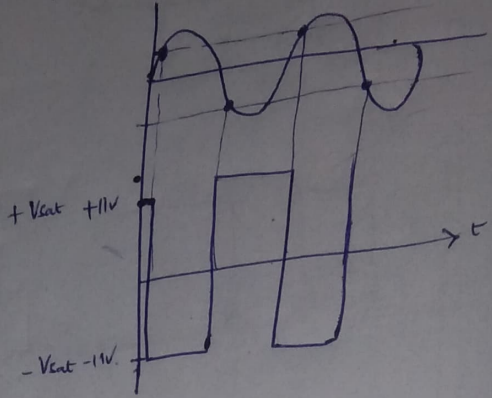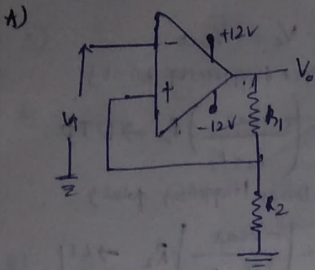supply of  $\pm 12V$ . Design ckt to have triggering



$$+V_{sat} = V_{cc} - 1 = 12 - 1 = 11V$$

$$-V_{sat} = -V_{cc} + 1 = -12 + 1 = -11V$$

$$\text{Let } I_2 = 100 I_{B_{max}} = (100 \times 500 \mu A)$$

$$I_2 = 50 \mu A$$

$$R_2 = \frac{2}{I_2}$$

$$= \frac{2}{50 \mu A}$$

$$R_2 = 40k\Omega$$

$$R_1 = \frac{11 - 2}{I_2}$$

$$R_1 = \frac{11 - 2}{50 \mu A}$$

$$R_1 = 180k\Omega$$

$$R_1 = 180k\Omega$$

$$R_2 = 39k\Omega$$

BIFET:

$$I_2 = 100 I_{B_{max}} = 50 \mu A$$



Choose  $R_1 = 1M\Omega$

$$I_2 = \frac{11 - 2}{1M\Omega} = \frac{V_o - V_f}{R_1} = 9 \mu A$$

$$R_2 = \frac{V_f}{I_2} = \frac{2}{9 \mu A} = 222.22k\Omega$$

$$R_2 = 220k\Omega$$

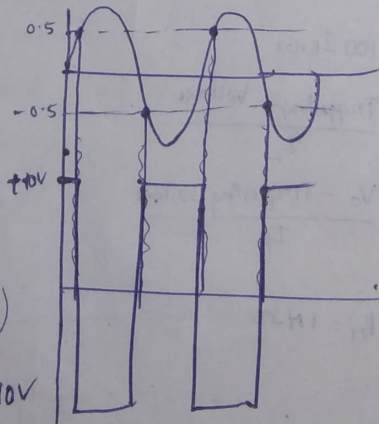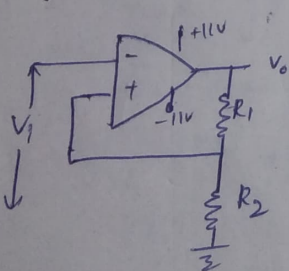② Using Bipolar op-amp design an inverting Schmitt trigger to trigger at  $\pm 0.5V$  to produce the o/p approximately  $\pm 11V$ .



$$+V_{sat} = V_{cc} - 1V = 11 - 1 = 10V$$

$$-V_{sat} = -V_{cc} + 1V = -11 + 1 = -10V$$



$$\text{Let } I_2 = 100 \text{ I}_{B\text{max}} \\ = (100)(500 \mu\text{A})$$

$$I_2 = 50 \mu\text{A}$$

$$R_2 = \frac{0.5}{I_2}$$

$$= \frac{0.5}{50 \mu\text{A}}$$

$$R_2 = 10 \text{ k}\Omega$$

$$B_1 = \frac{10 - 0.5}{I_2}$$

$$R_1 = \frac{10 - 0.5}{50 \mu\text{A}} = \frac{9.5}{50 \mu\text{A}}$$

$$R_1 = 190 \text{ k}\Omega$$

$$R_1 = 180 \text{ k}\Omega$$

③ Design an inv Schmitt trigger to have a tripping point of  $\pm 4 \text{ V}$  with a supply of  $\pm 15 \text{ V}$  using

① Bipolar op-amp

② BIFET op-amp

$$+V_{\text{sat}} = V_{\text{cc}} - 1 \text{ V} = 15 - 1 = 14 \text{ V}$$

$$-V_{\text{sat}} = -V_{\text{cc}} + 1 \text{ V} = -15 + 1 = -14 \text{ V}$$

$$V_T = \pm 4 \text{ V}$$

$$I_2 = 100 \text{ I}_{B\text{max}}$$

$$I_2 = 50 \mu\text{A}$$

$$R_2 = \frac{V_T}{I_2} = \frac{4 \text{ V}}{50 \mu\text{A}}$$

$$R_2 = 80 \text{ k}\Omega$$

$$R_2 = 68 \text{ k}\Omega$$

$$R_1 = \frac{+14 - 4 \text{ V}}{50 \mu\text{A}}$$

$$= 200 \text{ k}\Omega$$

$$R_1 = 180 \text{ k}\Omega$$

BIFET:

Choose  $R_1 = 1 \text{ M}\Omega$


$$B_1 = \frac{V_0 - V_{\text{Tripping}}}{I_2} \Rightarrow I_2 = \frac{V_0 - V_{\text{Tripping}}}{R_1}$$

$$I_2 = \frac{14 - 4}{1 \text{ M}\Omega}$$

$$I_2 = 10 \mu\text{A}$$


$$R_2 = \frac{V_T}{I_2} = \frac{4}{10 \mu\text{A}} = 400 \text{ k}\Omega$$

$$R_2 = 390 \text{ k}\Omega$$

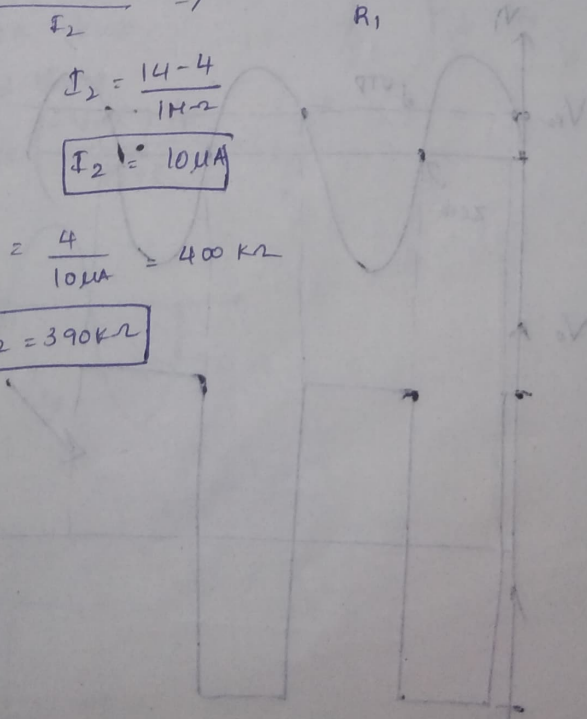

Asymmetrical Schmitt trigger:  
 Asymmetrical {UTP = -LTP}

Case: 1

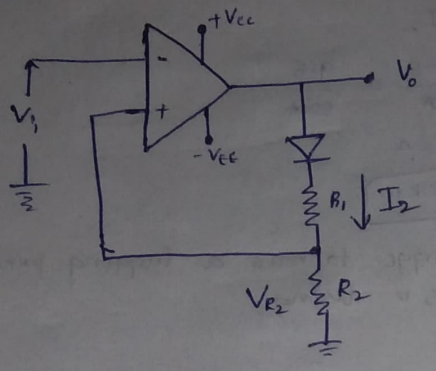

- Ckt diagram
- eqns
- waveforms
- Design

if  $V_i < V_{B2}$   $V_o = +V_{sat}$

When  $V_o = +V_{sat}$

Diode acts as forward bias } short cktly


$$V_{R2} = UTP = \left[ \frac{(+V_{sat} - V_F)}{B_1 + R_2} \cdot R_2 \right]$$

if  $V_i > V_{R2}$   $V_o = -V_{sat}$

When  $V_o = -V_{sat}$

Diode act as Reverse bias } open cktly

$$V_{R2} = 0.$$

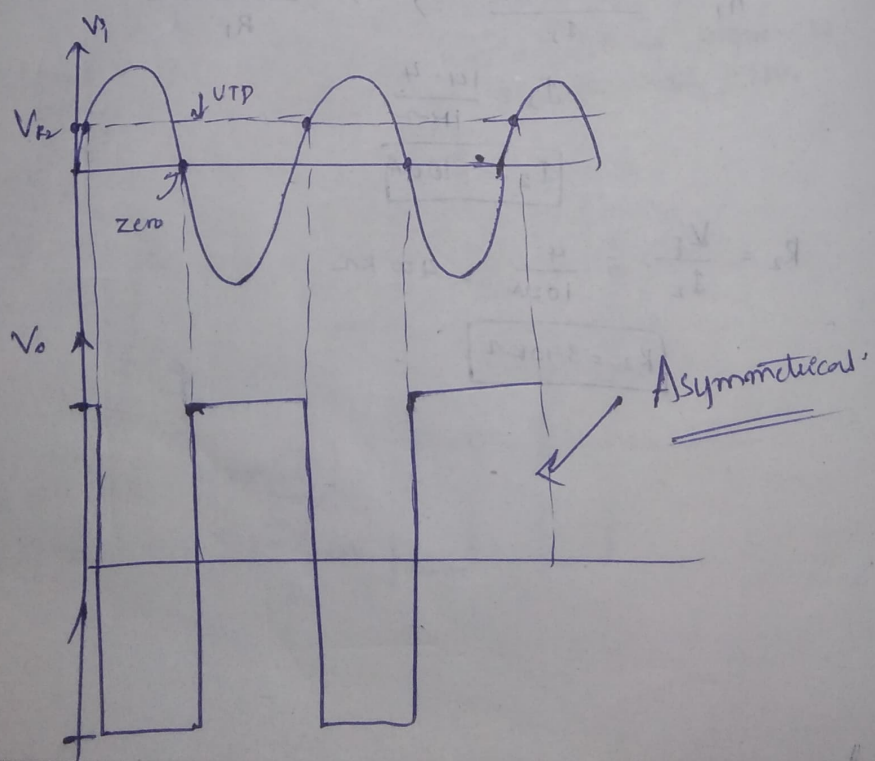

# Design:

1) 741 / Bipolar op-amp  
 Diode is there in ckt

then  $I_2 = 500 \mu A$

Choose current;

Bees to handle diode forward current

$$R_2 = \frac{V_{TP}}{I_2} \cdot \text{diff}$$

to find  $R_1$

$$V_{TP} = \frac{+V_{sat} - V_F}{R_1 + R_2} \cdot R_2 \quad \{ \text{find } R_1 \}$$


2) BIFET:

Choose  $R_1 = 1M \Omega$

to find  $R_2$  use  $V_{TP} = \left[ \frac{+V_{sat} - V_F}{R_1 + R_2} \cdot R_2 \right]$

## Case: 2

Now; Diode is Reversed.

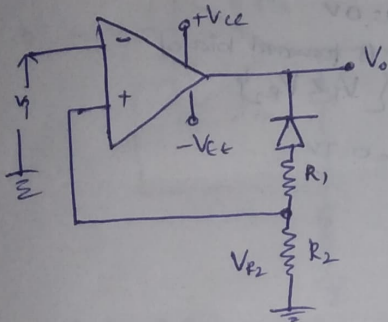

If  $V_i < V_{R_2}$   $V_o = +V_{sat}$


Diode: Reverse biased { open ckt }

$$V_{R_2} = 0$$

If  $V_i > V_{R_2}$   $V_o = -V_{sat}$

Diode: forward biased
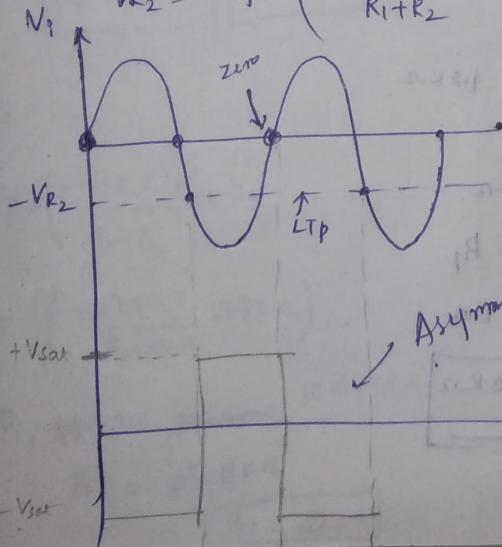
$$-V_{R_2} = LTP = \left( \frac{-V_{sat} + V_F}{R_1 + R_2} \cdot R_2 \right)$$



Design:

Since the diode is

\* Choose  $I_2 = 500 \mu A$

\*  $R_2 = \frac{LTP}{I_2}$


\*  $-V_{R_2} = LTP = \frac{(-V_{sat} + V_F) \times R_2}{R_1 + R_2}$  ← find  $R_1$

BIFET:

\* Choose  $R_1 = 1 M\Omega$

\* from  $-V_{R_2} = LTP = \left[ \frac{(-V_{sat} + V_F) \times R_2}{R_1 + R_2} \right]$  ← find  $R_2$

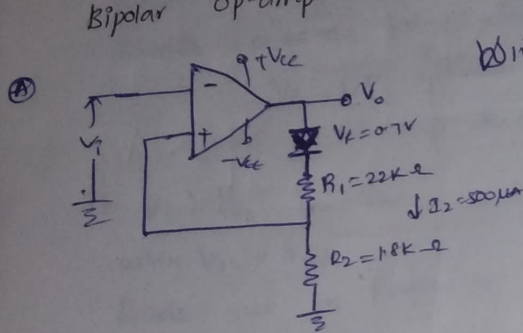① An inverting Schmitt trigger ckt is to have  $U_{TP} = 1V$  &  $LTP = 0V$  with  $\pm 15V$  supply. Design suitable ckt using Bipolar op-amp



Since  $U_{TP} = 1V$   
 $LTP = 0V$   
 Diode is forward biased  
 $\{V_i < V_{R_2}\}$   
 $V_F = 0.7V$

$I_2 = 500 \mu A$

$R_2 = \frac{U_{TP}}{500 \mu A} = \frac{1}{500 \mu A}$

$R_2 = 2K\Omega$

$R_2 = 1.8K\Omega$

$V_{sat} = V_{cc} - 1V = 14V$

$U_{TP} = \left( \frac{V_{sat} - V_F}{R_1 + R_2} \right) (R_2)$


(1) =  $\frac{(14 - 0.7)}{R_1 + 1.8K\Omega} \times 1.8K\Omega$


$23940 = R_1 + 1.8K\Omega$

$23.94K\Omega - 1.8K\Omega = R_1$


$R_1 = 22.14K\Omega$

$R_1 = 22K\Omega$

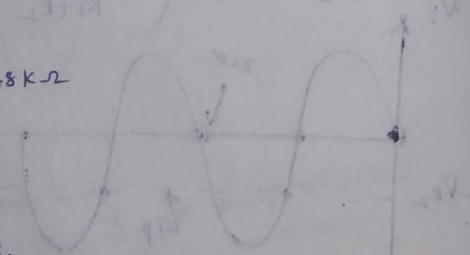

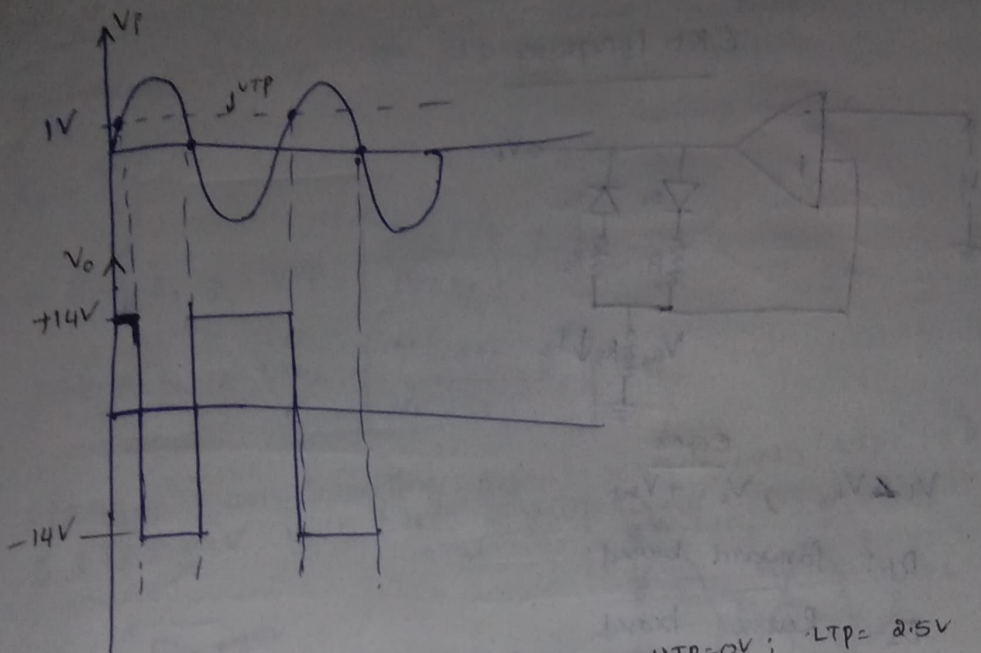

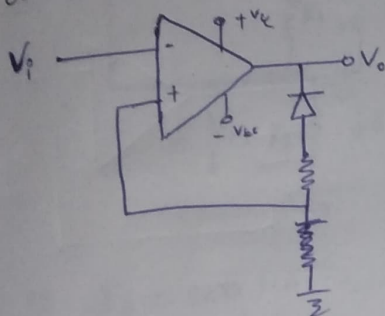Design a suitable CKT with power supply  $\pm 18V$ . with  $UTP = 0V$ ;  $LTP = 2.5V$ .  $\frac{1}{2}$  Bi-polar y



$$LTP = 2.5V$$

$$I_2 = 500\mu A$$

$$V_{cc} = +18V$$

$$R_2 = \frac{LTP}{I_2} = \frac{2.5V}{500\mu A}$$

$$R_2 = 5K\Omega \quad R_2 = 4.7K\Omega$$

$R_1$  : ?


$$LTP = \left( \frac{-V_{sat} + V_f}{R_1 + R_2} \right) \times R_2$$

$$2.5 = \left( \frac{-17 + 0.7}{R_1 + 4.7K\Omega} \right) \cdot 4.7K\Omega$$


$$R_1 = 30.644K\Omega$$

$$R_1 = 25.9K\Omega$$

$$R_1 = 22K\Omega$$

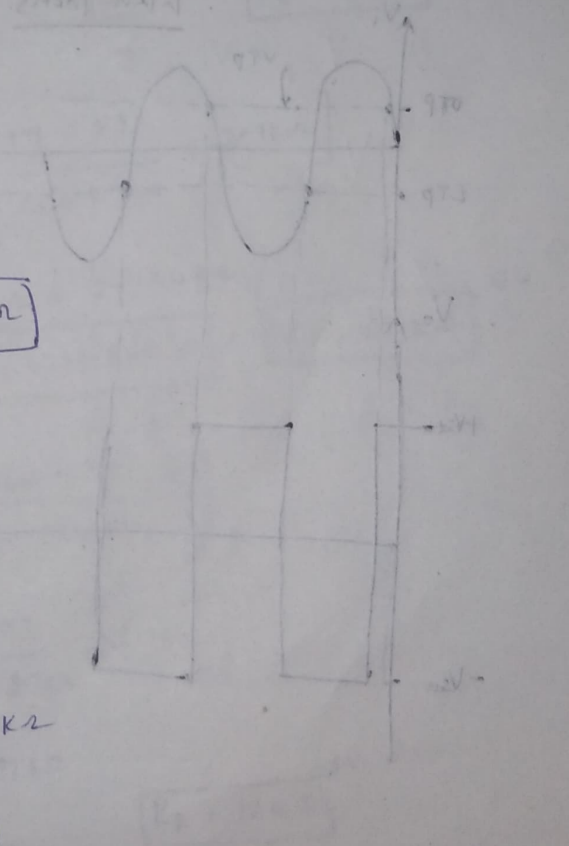

CKT Diagram

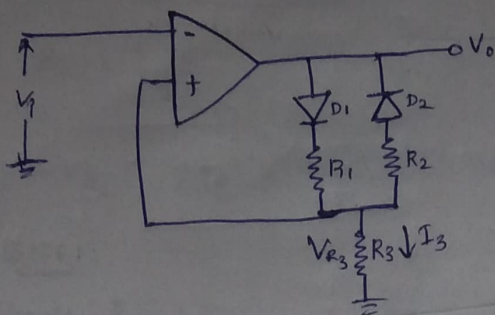

eqns

1)  $V_i < V_{R3}$ ,  $V_o = +V_{sat}$

$D_1$ : forward biased

$D_2$ : Reverse biased

$$V_{R3} = UTP = \left[ \frac{+V_{sat} - V_f}{R_1 + R_3} \cdot R_3 \right]$$


2)  $V_i > V_{R3}$ ,  $V_o = -V_{sat}$

$D_1$ : Reverse biased

$D_2$ : forward biased

$$-V_{R3} = LTP = \left[ \frac{-V_{sat} + V_f}{R_2 + R_3} \cdot R_3 \right]$$

WAVE FORMS

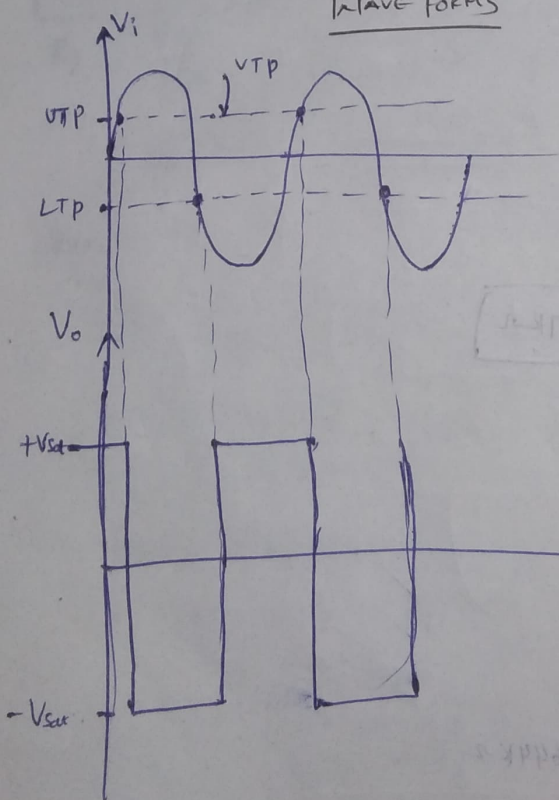

Handwritten notes and calculations on the right side of the page, including:

- $V_{R3} = 9.1V$
- $V_{sat} = 18V$
- $R_1 = 200\Omega$
- $R_2 = 200\Omega$
- $R_3 = 200\Omega$
- $V_f = 0.7V$
- $V_{TP} = \frac{18 - 0.7}{200 + 200} \cdot 200 = 9.1V$
- $V_{LTP} = \frac{-18 + 0.7}{200 + 200} \cdot 200 = -9.1V$

DESIGN :


\* Current through  $R_3$   $I_3 = 500 \mu A$

\*  $R_3 = \frac{UTP}{I_3}$

\* to find  $R_1 \Rightarrow UTP = \left[ \frac{V_{sat} - V_F}{R_1 + R_3} \cdot R_3 \right]$

\* to find  $R_2 \Rightarrow LTP = \left[ \frac{-V_{sat} + V_F}{R_2 + R_3} \cdot R_3 \right]$

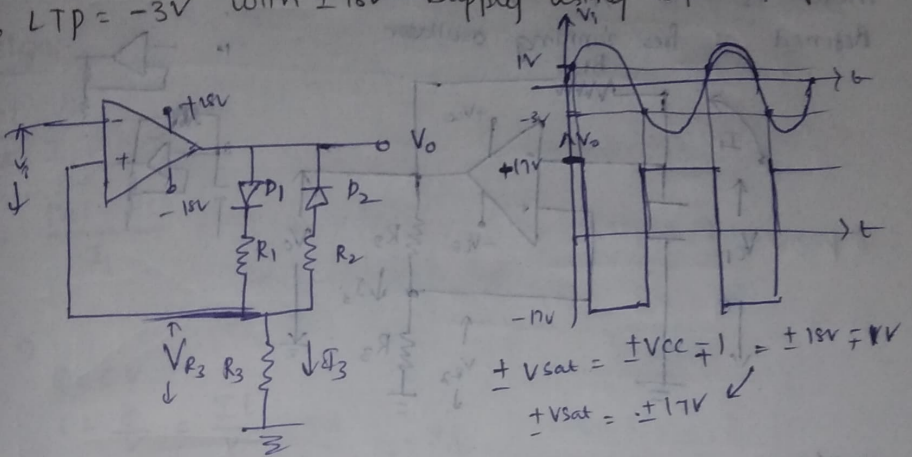① Design an inverting Schmitt trigger with  $UTP = 1.5V$  &  $LTP = -3V$  with  $\pm 18V$  supply using Bipolar opamp



1)  $I_3 = 500 \mu A$

2)  $R_3 = \frac{UTP}{I_3} = \frac{1.5V}{500 \mu A} = 3k\Omega$

$R_3 = 2.7k\Omega$

3)  $R_1 \Rightarrow 1.5V = \left[ \frac{17 - 0.7}{R_1 + 2.7k\Omega} \cdot 2.7k\Omega \right]$

$R_1 + 2.7k\Omega = 29.134k\Omega$

$R_1 = 26.64k\Omega$

$R_1 = 27k\Omega$

4)  $R_2 \Rightarrow LTP = \left[ \frac{-V_{sat} + V_F}{R_2 + R_3} \cdot R_3 \right]$

$3 = \left[ \frac{-17 + 0.7}{R_2 + 2.7k\Omega} \cdot 2.7k\Omega \right]$

$R_2 = 11.97k\Omega$

$R_2 = 12k\Omega$


3) MULTIVIBRATOR'S USING OP-AMP:-

- Astable MV { Also called Oscillator }
- Monostable MV
- Bistable MV

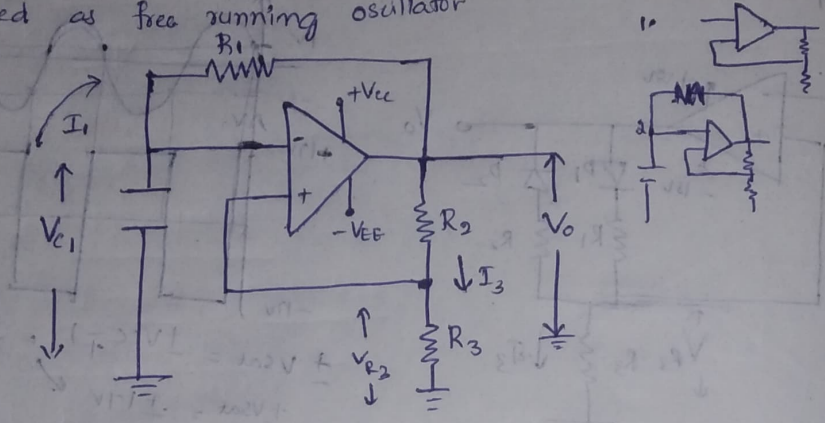50) ASTABLE MULTIVIBRATOR { using op-amp }

Astable multivibrator doesn't have any stable state the output always switches from one state to another state.

There is no external i/p for Astable Multivibrator, so it is defined as free running oscillator



working:

Voltage at inverting terminal is compared with voltage at non-inverting terminal.

if  $V_{C1} < V_{R3}$   $\Rightarrow V_o = +V_{sat} = V_{cc} - 1$

$$V_{R3} = UTP \frac{+V_{sat}}{R_2 + R_3} \cdot R_3$$


$V_{C1}$  compared with UTP; if  $V_{C1}$  crosses UTP; the o/p immediately jumps to  $-V_{sat}$

if  $V_{C1} > V_{R3}$   $\Rightarrow V_o = -V_{sat} = -V_{cc} + 1$

$$V_{R3} = LTP \frac{-V_{sat}}{R_2 + R_3} \cdot R_3$$



Waveform:

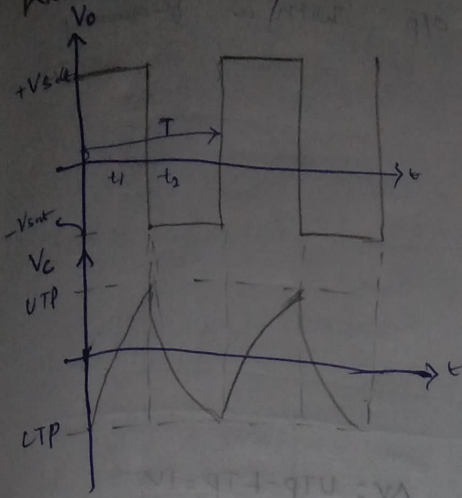

{ NO stable state  
o/p Always switches  
from one state to other state }

Design:-

\*)  $\frac{741}{\text{Let } I_1 = 100 I_{B \text{ Max}}}$

2)  $R_1 = \frac{|V_{o1}| - UTP}{I_1}$  { UTP; LTP are same }  
↑  
nothing but tripping voltage

3)  $C_1 \Rightarrow \Phi = CV$   
 $C = \frac{\Phi}{V} = \frac{I_1 t}{V}$   $t_1 = T/2$

$C_1 = \frac{I_1 t_1}{\Delta V}$  {  $\Delta V = UTP - LTP$  }

4) Let  $I_3 = 100 I_{B \text{ Max}}$

5)  $R_3 = \frac{V_{R3}}{I_3} = \frac{UTP}{I_3}$

(b)  $R_2 = \frac{|V_{o1}| - UTP}{I_3}$

\* BIFET / LF353 :-  $\downarrow$  (Imp)  
 { NO,  $I = 100 I_{B \text{ Max}}$  for BIFET }

1) Choose  $R_2 = 1M \Omega$

2)  $I_3 = \frac{|V_{o1}| - UTP}{R_2}$

3)  $R_3 = \frac{UTP}{I_3}$


4) Choose  $C_1 = 0.1 \mu F$  { TO avoid parasitic capacitance }

5)  $I_1 = \frac{C_1 \Delta V}{t_1}$

6)  $R_1 = \frac{|V_{o1}| - UTP}{I_1}$

(Imp)  
 \* If their combination of R and C; choose capacitor instead of resistor

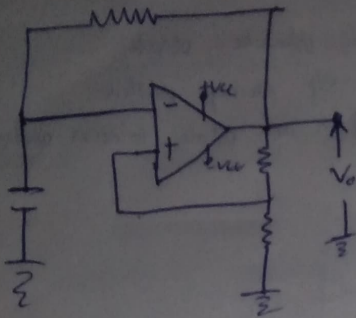(1) using a BIFET OP-AMP DESIGN A ASTABLE MULTIVIBRATOR to have  $\pm 9V$  o/p with a frequency of 1 kHz



$$\pm 9V = \pm V_{sat}$$

$$V_{sat} = 9V$$

$$V_{cc} = V_{sat} + 1$$

$$V_{cc} = 10V$$

Normally  $\Delta V = UTP - LTP = 1V$

$$UTP = 0.5$$

$$LTP = -0.5$$

1) Choose  $R_2 = 1M\Omega$

$$2) I_3 = \frac{9 - 0.5}{1M\Omega} = \frac{|V_o| - V_{UTP}}{R_2}$$

$$I_3 = 8.5 \mu A$$

$$3) R_3 = \frac{0.5}{I_3} = 58.82 K\Omega$$

$$R_3 = 56 K\Omega$$

4) choose  $C_1 = 0.1 \mu F$

$$5) I_1 = \frac{C_1 \Delta V}{t_1} = \frac{(0.1 \mu F)(1V)}{0.5 \text{ msec}}$$

$$I_1 = 0.2 \text{ mA}$$

$$6) R_1 = \frac{|V_o| - UTP}{I_1} = \frac{9 - 0.5}{0.2 \text{ mA}}$$

$$R_1 = 42.5 K\Omega$$

$$R_1 = 39 K\Omega$$

(2) Design an op-amp Astable Multivibrator to have o/p frequency 400Hz use a 741 op-amp with a supply of  $\pm 18V$ .

$$f = 400 \text{ Hz}$$

$$V_{cc} = +18V$$

$$T = 2.5 \text{ msec}$$

$$t_1 = 1.25 \text{ msec}$$

$$V_{sat} = 17V$$

$$I_1 = 100 I_{Bmax} = 50 \mu A$$

$$R_1 = \frac{|V_0| - V_{TP}}{I_1} = \frac{17 - 0.5}{50 \mu A}$$

$$R_1 = 330 k\Omega$$

$$C_1 = \frac{I_1 t_1}{\Delta V}$$

$$= \frac{(50 \mu A)(1.25 \text{ msec})}{1V}$$

$$C_1 = 0.06 \mu F$$

$$I_3 = 100 I_{Bmax} = 50 \mu A$$

$$R_3 = \frac{V_{TP}}{I_3} = \frac{0.5}{50 \mu A}$$

$$R_3 = 10 k\Omega$$

$$R_2 = \frac{|V_0| - V_{TP}}{I_3} =$$

$$R_2 = 330 k\Omega$$

### BIFET

1) Choose  $R_2 = 1M\Omega$

$$I_3 = \frac{|V_0| - V_{TP}}{R_2} = \frac{17 - 0.5}{1M\Omega} = 16.5 \mu A$$

$$R_3 = \frac{V_{TP}}{I_3} = 30.3 k\Omega$$

$$R_3 = 27 k\Omega$$

4) Choose  $C_1 = 0.1 \mu F$

$$I_1 = \frac{C_1 \Delta V}{t_1} = \frac{(0.1 \mu F)(1V)}{1.25 \text{ msec}} = 0.08 \text{ mA}$$

$$R_1 = \frac{|V_0| - V_{TP}}{I_1} = 206.25 k\Omega$$

$$R_1 = 180 k\Omega$$

Design Astable multivibrator using 741 opamp  
with  $\pm 15V$  supply with  $T_{on} = T_{off} = 1ms$ .

1) Choose  $I_1 = 100 I_{Bmax}$

$$I_1 = 50 \mu A$$

2) 
$$R_1 = \frac{|V_{ol}| - UTP}{I_1}$$

$$= \frac{14 - 0.5}{50 \mu A}$$

$$R_1 = 270K \Omega$$

$$V_o = +V_{cc} - 1$$

$$= 15 - 1 = 14V$$

$$V_{sat} = 14V$$

if UTP, LTP,  $\Delta V$  not mentioned  
consider UTP = 0.5V; LTP = -0.5V;  $\Delta V = 1V$

3) 
$$C_1 = \frac{I_1 t_1}{\Delta V}$$

$$= \frac{(50 \mu A)(1ms)}{1V}$$

$$C_1 = 50 nF$$

$$C_1 = 0.05 \mu F$$

4)  $I_3 = 100 I_{Bmax} = 50 \mu A$

5) 
$$R_3 = \frac{UTP}{I_3} = \frac{0.5}{50 \mu A}$$

$$R_3 = 10K \Omega$$

6) 
$$R_2 = \frac{|V_{ol}| - UTP}{I_3} = \frac{14 - 0.5}{50 \mu A}$$


$$R_2 = 270K \Omega$$

# MONOSTABLE MULTIVIBRATOR USING OP-AMP:-




Monostable multivibrator has one stable state. If it stays in stable state until trigger is applied.

When trigger input is applied it switches to the opposite state for a time dependent on the circuit components.

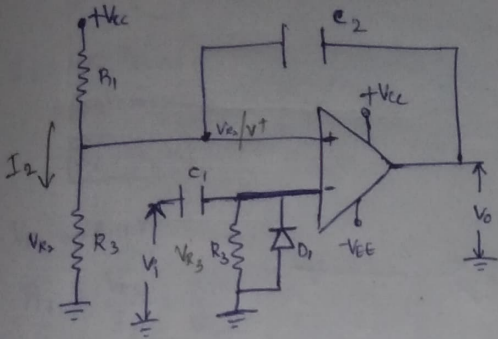{ Similar to capacitor coupled crossing detectors with some modifications }



Feedback Capacitor  $C_2$   
Diode (D1)

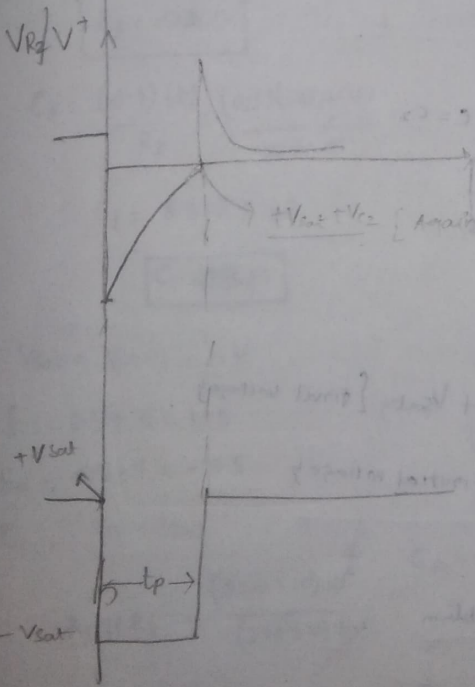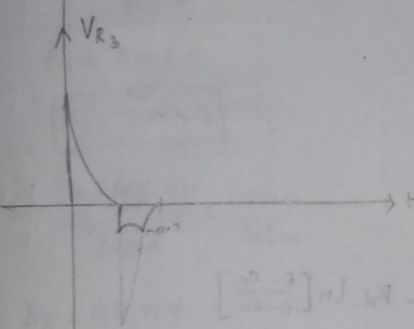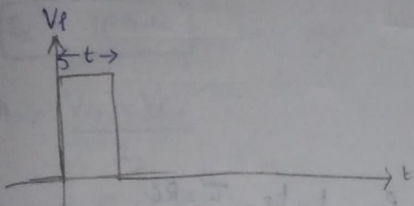


{ No need of negative supply  
so Diode & capacitor  
Circuit }

## Design:-

T41:-

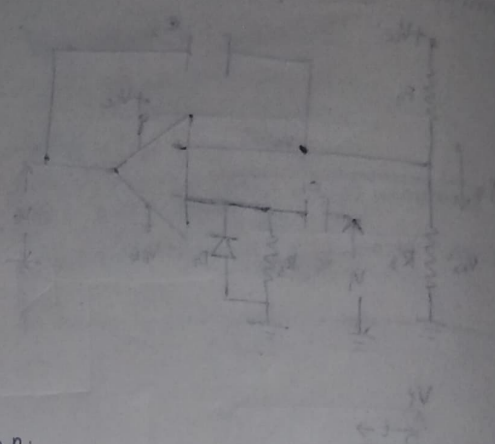- 1) Let  $I_2 = 100 I_{Bmax}$
- 2)  $V_{R_2} = 0.5V$  } Assume  $I_2$
- 3)  $R_2 = \frac{V_{R_2}}{I_2}$
- 4)  $R_1 = \frac{+V_{cc} - V_{R_2}}{I_2}$
- 5)  $R_3 = \frac{0.1 V_{BE}}{I_{Bmax}}$
- 6)  $C_1 R_3 = 0.1 t$   
 $C_1 = \frac{0.1 t}{R_3}$



7) To find  $C_2$   
Consider Capacitor Charging eq<sup>n</sup>:

$$V_c(t) = V_F - [V_F - V_I] e^{-t/\tau}$$

Let  $V_F = E$ ,  $V_I = E_0$  and  $V_c(t) = e_c$ ,  $t = t_p$ ,  $\tau = RC$

$$e_c = E - [E - E_0] e^{-t_p/RC}$$

$$E - e_c = (E - E_0) e^{-t_p/RC}$$

$$e^{-\frac{t_p}{RC}} = \frac{E - e_c}{E - E_0}$$

$$\frac{t_p}{RC} = \ln \left[ \frac{E - e_c}{E - E_0} \right] \quad t_p = -RC \ln \left[ \frac{E - e_c}{E - E_0} \right]$$

$$t_p = RC \ln \left[ \frac{E - E_0}{E - e_c} \right]$$

$t_p$ : pulsewidth  $R = R_1 || R_2$   $C = C_2$

$$t_p = (R_1 || R_2) C_2 \ln \left[ \frac{E - E_0}{E - e_c} \right]$$

$$C_2 = \frac{t_p}{(R_1 || R_2) \ln \left[ \frac{E - E_0}{E - e_c} \right]}$$

$$E = V_F = V_{R_2} - [-V_{sat}] = V_{R_2} + V_{sat} \text{ } \{ \text{final voltage} \}$$

$$E_0 = V_{R_2} + [-V_{sat}] = V_{R_2} - V_{sat} \text{ } \{ \text{initial voltage} \}$$

$$e_c = 0 - (-V_{sat}) = V_{sat}$$

{ voltage across capacitor when switch is bitum  
 $-V_{sat}$  to  $+V_{sat}$  }

Design Monostable Multivibrator to have an o/p pulse width of 1msec when triggered by 2V, 100µsec 1/p pulse use 741 op amp with ±12V supply!

- ①
- $t_p = 1 \text{ msec}$
  - $t = 100 \mu\text{sec}$
  - $V_i = 2 \text{ V}$
  - $V_{cc} = +12 \text{ V}$

1)  $I_2 = 100 I_{B \text{ Max}}$   
 $= (100)(500 \text{ nA})$   
 $I_2 = 50 \mu\text{A}$

2)  $V_{R2} = 0.5 \text{ V}$

3)  $R_2 = \frac{V_{R2}}{I_2} = \frac{0.5}{50 \mu\text{A}}$

$R_2 = 10 \text{ K}\Omega$

4)  $R_1 = \frac{V_{cc} - V_{R2}}{I_2}$   
 $= \frac{12 - 0.5}{50 \mu\text{A}}$

$R_1 = 230 \text{ K}\Omega$

$R_1 = 220 \text{ K}\Omega$

5)  $R_3 = \frac{(0.1)(10^{-7})}{50 \text{ nA}} = \frac{0.1 V_{cc}}{50 \text{ nA}}$

$R_3 = 140 \text{ K}\Omega$

$R_3 = 120 \text{ K}\Omega$

6)  $C_1 = \frac{(0.1)(t)}{R_3} = \frac{(0.1)(100 \mu\text{sec})}{120 \times 10^3}$

$C_1 = 83.33 \text{ pF}$

$C_1 = 91 \text{ pF}$

7)  $V_{\text{sat}} = V_{cc} \Rightarrow 11 \text{ V}$

$E = 0.5 + 11 = 11.5$

$E_0 = 0.5 - 11 = -10.5$



$E_c = 11 \text{ V} = V_{\text{sat}}$

$R_1 \parallel R_2 = \frac{(220 \times 10^3)^2}{(220 + 10) \times 10^3}$

$C_2 = \frac{t_p}{(R_1 \parallel R_2) \ln \left[ \frac{E - E_0}{E - E_c} \right]}$

$C_2 = \frac{1 \text{ msec}}{(9.5652 \times 10^3) \ln \left[ \frac{11.5 + 10.5}{11.5 - 11} \right]}$

$C_2 = 0.027 \mu\text{F}$

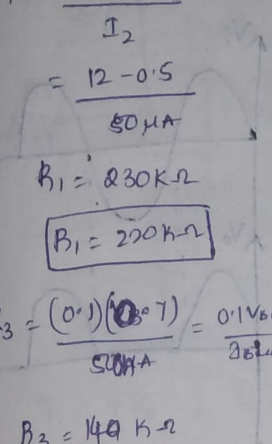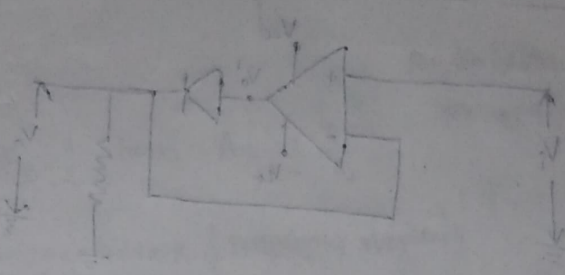


# Signal processing circuits:-

## 1) precision Rectifier

### ① precision Rectifier:-


- precision rectifier are those circuits which rectify the signals whose voltage is less than 0.7 volts
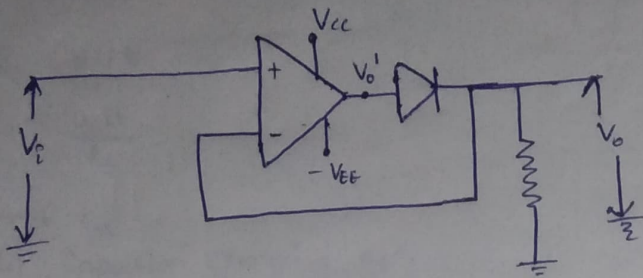
#### a) precision halfwave rectifier; {using voltage follower}



1) if  $V_i = +ve$  ;  $V_o' = +ve$   
 Diode: forward biased  
 $V_o = V_i$

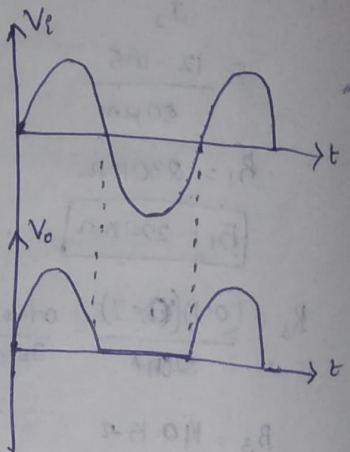2) if  $V_i = -ve$  ;  $V_o' = -ve$   
 Diode: Reverse biased  
 {open ckt}  
 $V_o \text{ o/p } \Rightarrow V_o = 0 \text{ volts}$




↳ Also known as saturating precision Halfwave Rectifier.

Adv: \* Amplifies <sup>below</sup>  $V_T$ .

- 1) provide gain to o/p
- 2) no diode drop
- 3) Acts ideal diode ckt  
 {op-amp: low o/p impedance}
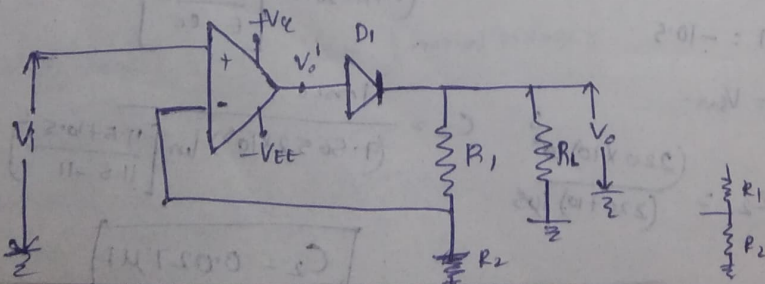
#### b) Saturating precision HWR {using non-inverting Amplifier}






if  $V_i = +V_e$ ,  $V_o^+ = +V_e$   
 Diode: forward biased

$$\frac{V_o}{V_i} = A_{Vf}$$

$$V_o = \left(1 + \frac{B_1}{R_2}\right) V_i$$

if  $V_i = -V_e$ ,  $V_o^+ = -V_e$   
 Diode: Reverse biased

$$V_o = 0 \text{ volts}$$

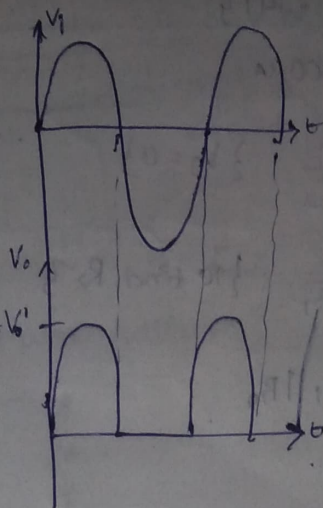

Note:  
 diode can be reversed.  
 ↓  
 o/p wave will be inverted

Design:-


$$I_2 = 500 \mu A$$

$$R_2 = \frac{V_i}{I_2}; R_1 = ? \text{ from } A_{Vf} = 1 + \frac{B_1}{R_2}$$

for amplifier

o/p wave going

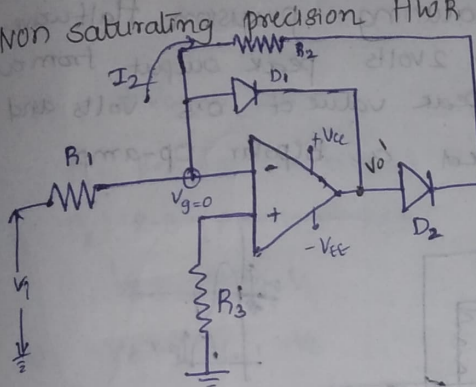c) Non saturating precision HWR { Inverting Amplifier }



$$R_s = R_1 // R_2$$

→  
 Biasing Resistor

$V_o^+ = -V_i$   
 If no diode  $V_o^+ = -V_e$   
 also: diode cut

if  $V_i = +V_e$ ,  $V_o^+ = -V_e$

$D_1$ : forward biased

$D_2$ : Reverse biased

$$V_o^+ = -0.7 \text{ volts}$$

When  $V_i = -V_e$ ,  $V_o^+ = +V_e$

$D_1$ : Reverse biased

$D_2$ : forward biased


$$V_o = \frac{-R_2}{R_1} V_i$$

$$\text{At } R_2 = R_1$$

$$V_o = -V_i$$

$$\text{But } V_i = -V_e$$

$$V_o = +V_e$$

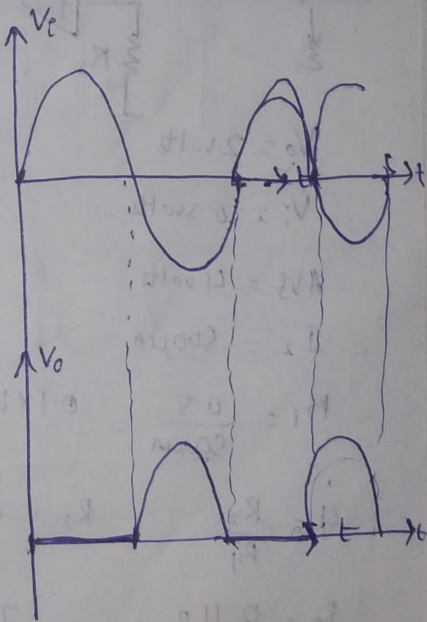

$$R_2 > R_1$$

Amplification is provided

Design :- {741}

$$I_2 = 500 \mu A$$

$$R_2 = \frac{V_1}{I_2} \quad \{V_0 = 0\}$$

$$A_v = \frac{R_2}{R_1} \quad \{ \text{to find } R_2 \}$$

$$R_3 = R_1 \parallel R_2$$

{ BIFET }


1)  $R_2 = 1M \Omega$

2)  $R_1$  { from  $A_v = R_2/R_1$  }

3)  $R_3 = R_1 \parallel R_2$

(1) Design a non-saturating precision half-wave rectifier to produce a 2 volts peak output from a sine wave 1/p with a peak value of 0.5 volts and frequency of 1MHz? Use a Bipolar Op-amp with supply  $\pm 15V$ .

(A)

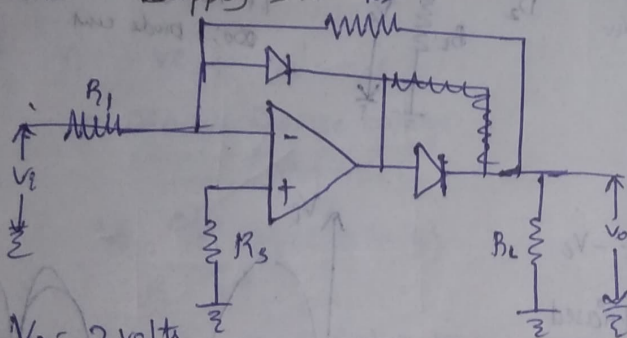

$$\frac{V_0}{V_i} = \frac{2}{0.5} = 4$$

$V_0 = 2 \text{ volts}$

$V_i = 0.5 \text{ volts}$

$A_v = 4 \text{ volts}$

$I_2 = 500 \mu A$

$R_1 = \frac{0.5}{500 \mu A} = 0.1 \times 10^4 = 1K \Omega$   $R_1 = 1K \Omega$

$4 = \frac{R_2}{R_1}$   $R_2 = 4K \Omega$   $R_2 = 3.9K \Omega$

$R_3 = R_1 \parallel R_2 = 795.91 \Omega$


$R_3 = 820 \Omega$

Note: Breakdown voltage of diodes  $D_1$  and  $D_2$  should be greater than 30 volts  $\{+15 - (-15)\}$  supply  $\pm 15$ .

Therefore reverse recovery time of diode should be less than "T" (TRR)

let  $T_{rr} = \frac{1}{10} T$   $T \Rightarrow \frac{1}{f} = \frac{1}{1 \text{ MHz}} = 10^{-6} \text{ sec} = 1 \mu\text{sec}$

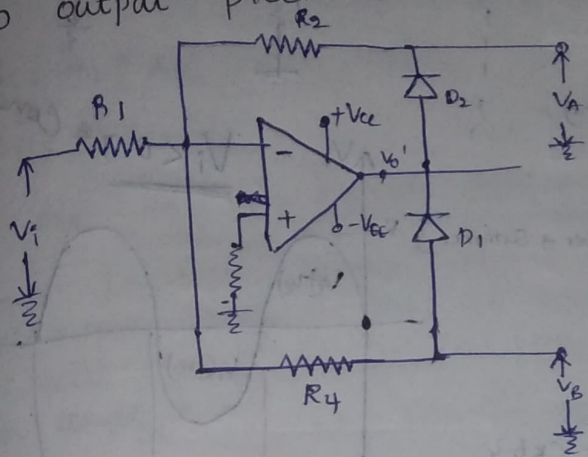d) Two output precision half wave rectifiers -



$V_i = +V_e ; V_0' = -V_e$

$D_1$ : f.B {forward biased}

$D_2$ : R.B {Reverse biased}



$V_B = -R_4/R_1 V_i$

$V_i = -V_e ; V_0' = +V_e$

$D_1$ : R.B


$D_2$ : f.B

$V_A = -R_2/R_1 V_i$

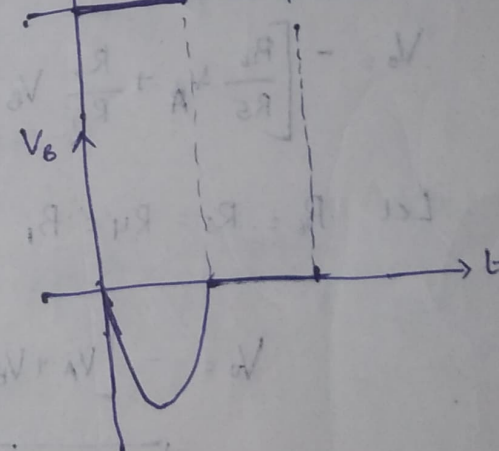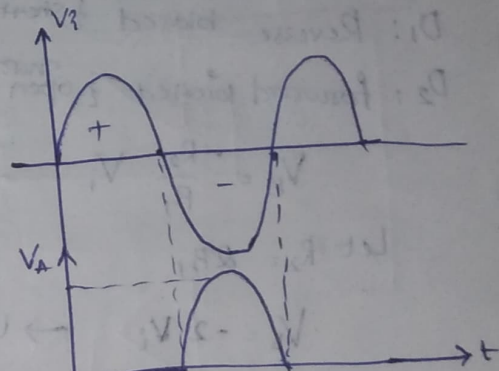


$V_0 = V_i$

# FULL WAVE PRECISION RECTIFIER

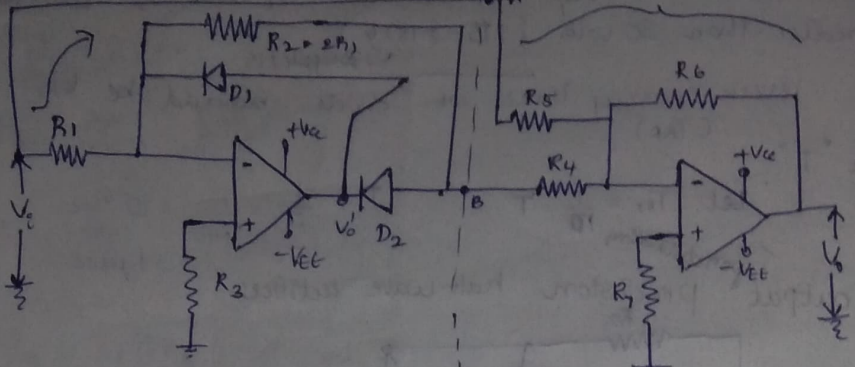

Non-saturating Inverting Amplifier

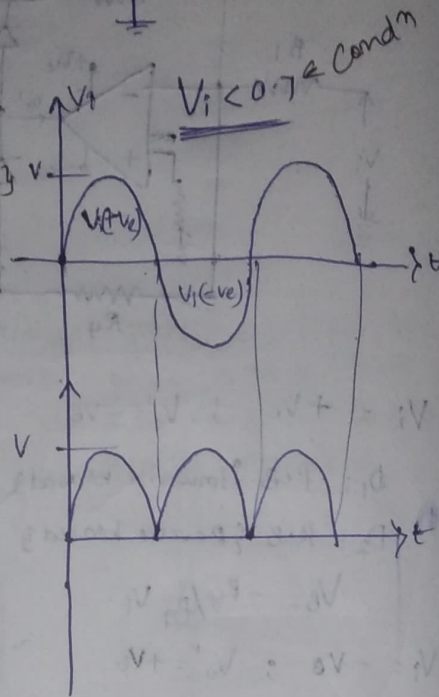HWR  
 { non-saturating Inverting Amplifier + Summer }



Case (i)

$V_i = +ve ; V_o' = -ve$

$D_1$ : Reverse biased { open short ckt }

$D_2$ : forward biased { short open ckt }

$$V_B = -\frac{R_2}{R_1} V_i$$

Let  $R_2 = 2R_1$

$$V_B = -2V_i \rightarrow (1)$$

$$V_o = -\left[ \frac{R_6}{R_5} V_A + \frac{R_6}{R_4} V_B \right]$$

Let  $R_6 = R_5 = R_4 = R_1$

$$V_o = -[V_A + V_B] = -[V_i - 2V_i]$$

$V_o = V_i$

Summing Amplifier

since  $V_A = V_i$  &  $V_B = -2V_i$  { from (1) }


Case (ii)

$V_i = -ve ; V_o' = +ve$

$D_1$ : forward biased ;  $D_2$ : Reverse biased  
 (short ckt) { open ckt }

$V_B = 0 ; V_A = V_i = -V_i$

{ short ckt } given negative  $V_i$

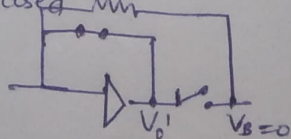

$$V_o = - \left[ \frac{R_6}{R_3} V_A + \frac{R_6}{R_4} V_B \right]$$

$$R_6 = R_5 = R_4 = R_1$$

$$V_o = - [V_A + V_B]$$

$$V_o = - [-V_i] = +V_i$$

$$R_3 = R_1 \parallel R_2$$

$$R_7 = R_4 \parallel R_5 \parallel R_6$$

ckt also called as

Absolute value ckt

Q1 Design precision fullwave Rectifier ckt to produce a 2 volts peak output from a sine wave input with a peak value of 0.5 volts and a frequency of 1MHz use a bipolar opamp with supply  $\pm 15V$ ?

- Non-saturation o/p
- $V_{cc} = +15V$

When diodes present in ckt  $I = 500 \mu A$

•  $V_o = 2 \text{ Volts}$

•  $V_i = 0.5 \text{ volts}$

$I_1 = 500 \mu A$

$R_1 = \frac{V_i}{I_1} = 1 \text{ k}\Omega$

$R_2 = 2R_1 = 2 \text{ k}\Omega$

$R_4 = R_5 = R_1 = 1 \text{ k}\Omega$  {choose}

$A_{Vf} = R_6/R_5$

$4 = R_6/1 \text{ k}\Omega$

$R_6 = 3.9 \text{ k}\Omega$

$R_3 = R_1 \parallel R_2 = \frac{(1 \text{ k}\Omega)(2 \text{ k}\Omega)}{1+2 \text{ k}\Omega} = \frac{2 \text{ k}\Omega}{3} = 666.6 \Omega = 680 \Omega$

$R_3 = 680 \Omega$

$R_7 = R_4 \parallel R_5 \parallel R_6$

$1 + 1 + \frac{1}{3.9}$


$\frac{1}{R_7} = \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6}$

$\frac{1}{R_7} = 2.25 \times 10^{-3}$

$\frac{1}{R_7} = \frac{2}{3} \text{ k}\Omega$

$448.18 \Omega = R_7$

$R_7 = 390 \Omega$

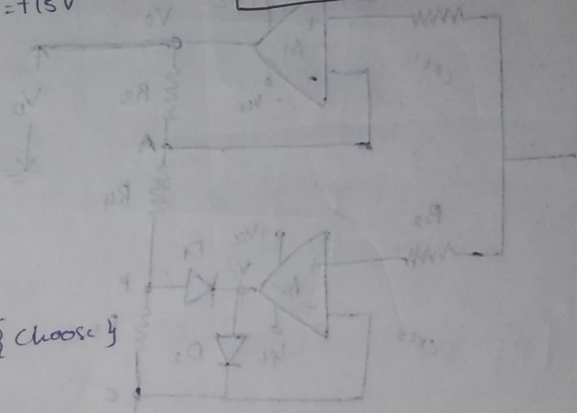

Notes:

1) Both diodes should maintain breakdown voltage greater than 20V }  $\pm 15V$  supply

2)  $T_{rr} = \text{reverse recovery time} = \frac{1}{10} T$



$f = 1 \text{ MHz} \quad T = 10^{-6} \text{ sec}$

$T_{rr} = 10^{-7} \text{ sec} = 0.1 \mu\text{sec}$

Drawback

input impedance is very low:  
as i/p is inverting Amplifier  
{ i/p  $Z = R_1$  } due to virtual ground.

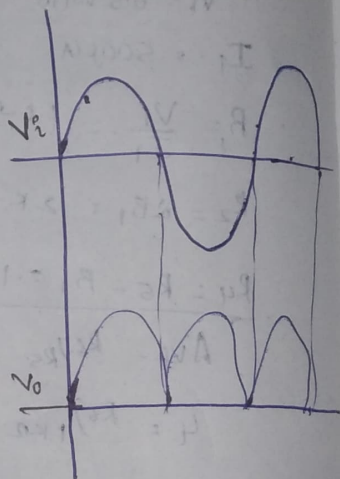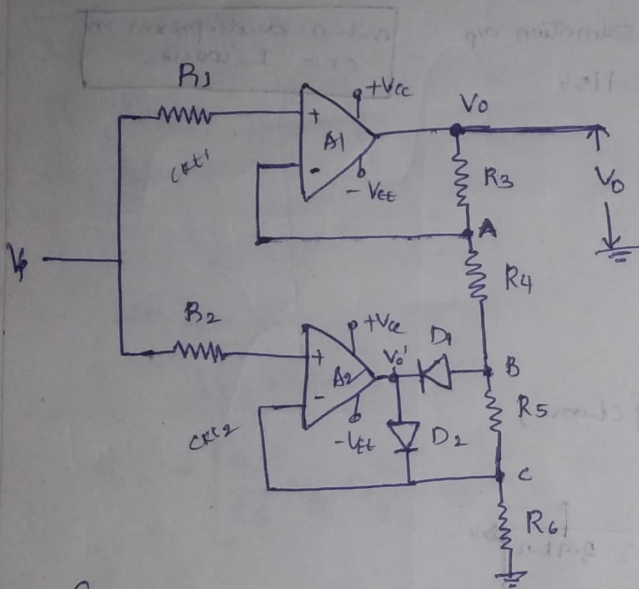High i/p impedance full wave precision Rectifier:



Case (i):

$V_i = +V_e$  ;  $V_A = V_i$ ,  $V_B = 0$ ,  $V_C = V_i$  } voltage follower  
ckt 2

$D_1$ : Reverse biased

$A_2$ : voltage follower

$D_2$ : forward biased

$V_A = V_i$  ;  $V_C = V_i$

No current flow through  $R_3, R_4, R_5, R_6$

Therefore  $V_o = V_i$

Case (ii)

$V_i = -V_e$  ;  $V_o' = -V_e$

$D_1$ : forward biased

$D_2$ : Reverse biased

A<sub>2</sub>: non-inverting amplifier

$$V_B = \left(1 + \frac{R_5}{R_6}\right) V_i$$

Let  $R_5 = R_6$

$$V_B = 2V_i \quad \text{since } V_i = -V_e$$

$$V_B = 2V_i \quad \text{--- (1)}$$

B) Superposition theorem  $\{V_0 = V_{01} + V_{02}\}$

Let i/p for A<sub>1</sub> = 0

$$V_{01} = +2V_i \left(\frac{R_3}{R_4}\right) = -R_3/R_4 V_B$$

$$R_3 = 2R_4 \quad \text{choose } R_4$$

$$V_{01} = 4V_i \quad \text{--- (2)}$$

Let i/p for A<sub>2</sub> = 0

$$V_{02} = 0$$

for A<sub>1</sub>  $\left\{ \begin{array}{l} \text{non-inverting amplifier} \\ \text{inverting terminal is zero} \\ \text{i/p at non-inverting terminal} \end{array} \right.$

$$V_{02} = \left(1 + \frac{R_3}{R_4}\right) V_i$$



we choose  $R_3 = 2R_4$

$$V_{02} = (1 + 2)V_i = 3V_i \quad \text{--- (3)}$$

from superposition theorem

$$V_0 = 4V_i - 3V_i = V_i$$

$$V_0 = V_i$$

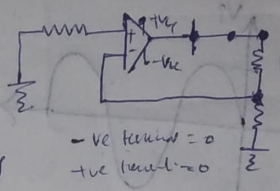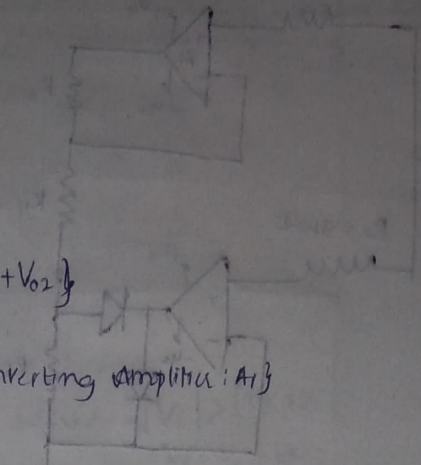

(Q1) Using Bipolar opamp with  $V_{cc} = \pm 15V$ , Design the high precision full wave rectifier circuit with the input peak voltage is to be 1V and no amplification to occur!

Draw wave forms & opt also

(A)  $I_B = 500\mu A$   $\left\{ \begin{array}{l} \text{due to presence of diodes} \end{array} \right.$

$$R_6 = \frac{V_i}{I_B} = \frac{1}{500\mu A} = \frac{10^6}{500} = 20k\Omega \Rightarrow R_5 = R_6$$

Let  $R_4 = R_6 = R_5 = 1.8k\Omega$

$$R_3 = 2R_4 = 3.6k\Omega$$

$$R_1 = R_3 \parallel R_4 = \frac{(3.6)(1.8)}{3.6 + 1.8} = 1.06k\Omega$$


$$R_2 = R_5 \parallel R_6 = \frac{(1.8)(1.8)}{1.8 + 1.8} = 0.9k\Omega$$

$$R_3 = 3.3k\Omega$$


$$R_1 = 1k\Omega$$

$$R_2 = 820\Omega$$

**CKT**


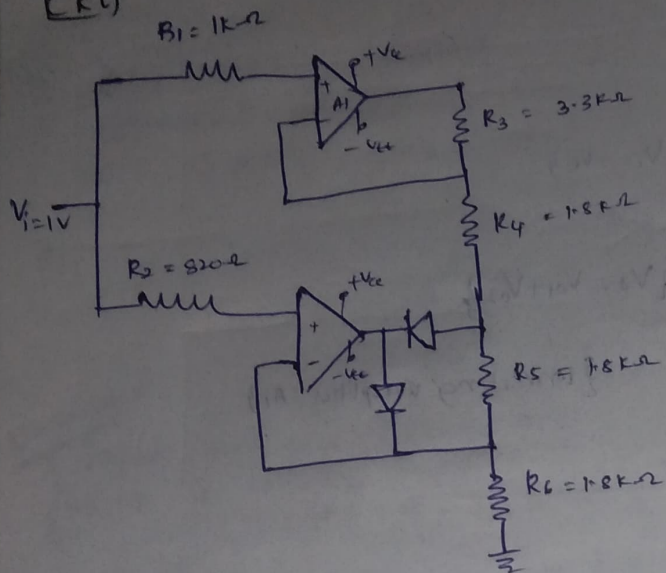


Wave forms:

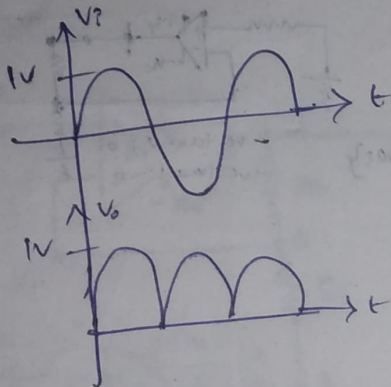



LIMITING CIRCUITS:-

(i) peak Clippers:-

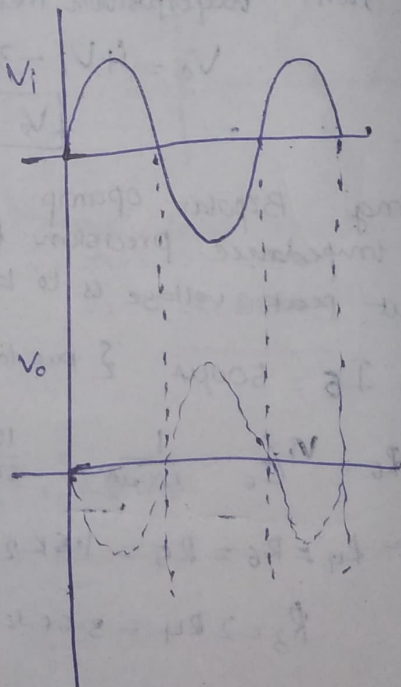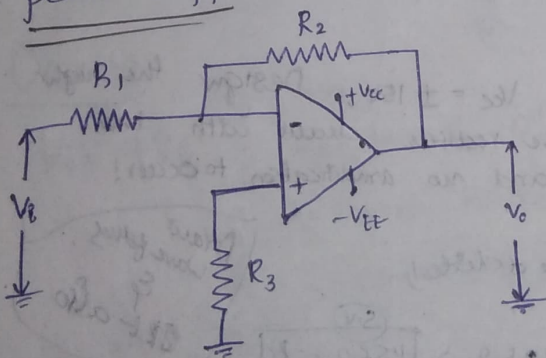



if Zener diodes connected back to base

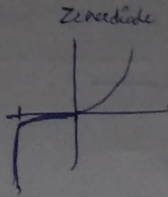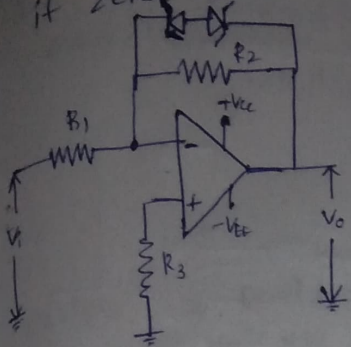

$V_Z$ : Zener diode voltage  
 $V_F$ : forward bias voltage

(1)  $V_i = +V_e, V_o = -V_e$

$D_1$ : Reverse bias  
 $D_2$ : forward bias


enter to breakdown  $|V_i| > (V_Z + V_F)$   
 Until  $V_Z + V_F, V_o = V_i$

$(V_Z + V_F)$

(2)  $V_i = -V_e, V_o = +V_e$

$D_1$ : fB;  $D_2$ : RB


Until  $V_Z + V_F, V_o = V_i$   
 $|V_i| > (V_Z + V_F), V_o = V_Z + V_F$

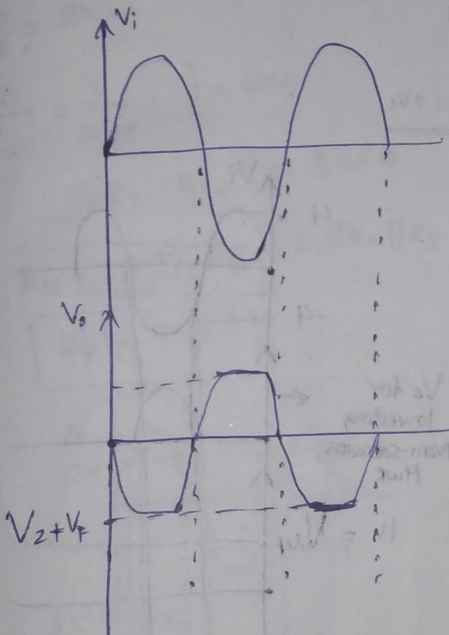


{ practice numerical }

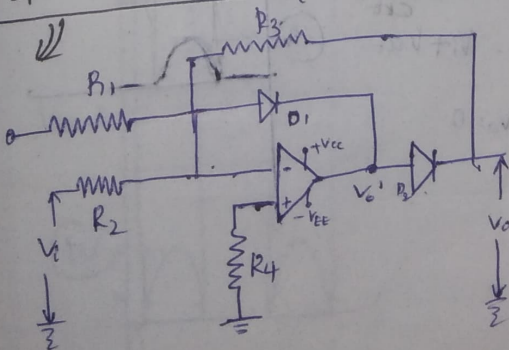(a) Dead zone circuit:

Modification of non-saturating HWR - clipping



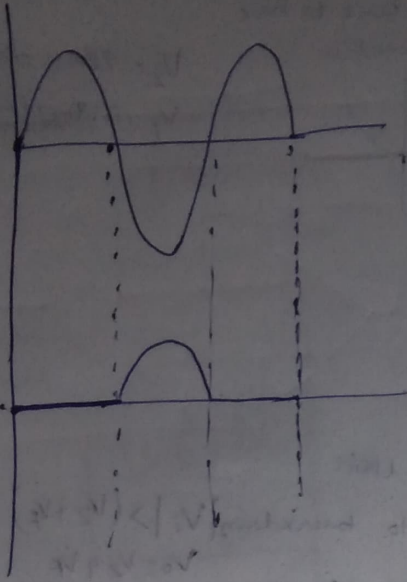

$V_i: +ve$   
 $D_1: FB; D_2: RB$

$V_o: \bullet$

$V_i: -ve$   
 $D_1: RB; D_2: FB$

$$V_o = -V_i = -(-V_i) = V_i$$

for inverting non-saturating HWR.

② for Dead zone ckt:  $V_{ref}: +ve$

$V_i: +ve; V_{ref} = IV$

$V_o: -ve$

$D_1: forward biased$

$D_2: Reverse biased$

$V_o = Zero$

if  $V_i: -ve; V_{ref} = IV$

$V_o: +ve$

$D_1: RB$

$D_2: FB$


$V_o$  if  $|V_i| > V_{ref} \quad V_o = V_i + V_{ref}$

$V_o$  if  $|V_i| \leq V_{ref} \quad V_o = 0$

$V_o$  for  
 Inverting  
 Non-saturating  
 HWR

$$IV = V_{ref}$$

for  
 Deadzone  
 ckt

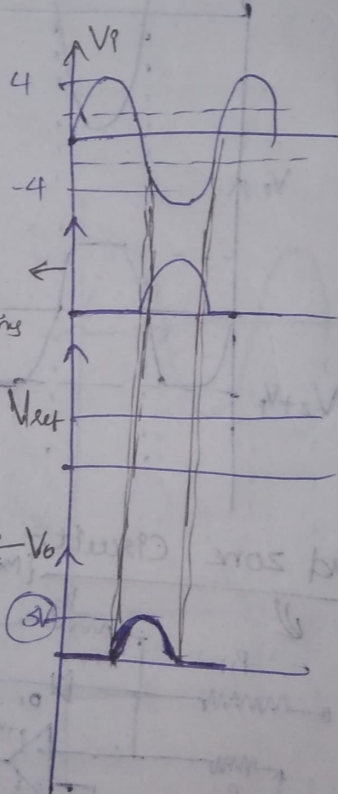


Design

alone as non-saturating inverting amplifier

$$R_4 = R_2 \parallel R_3 \parallel R_1$$

Design a Deadzone circuit to pass only upper 1/3rd portion of the +ve half cycle of the sine wave of input with peak value of 3V!

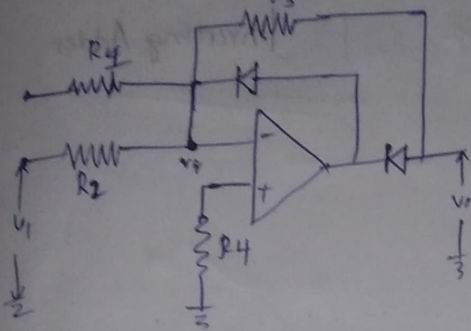She need to get o/p = 1V  
 $V_{act} = 2V$   $V_i = 3V$




$$I_2 = 500\mu A$$

$$R_2 = \frac{V_i}{I_2} = \frac{3}{500\mu A} \} = 6K\Omega$$


$$R_2 = R_1 = R_3 = 5.6K\Omega$$

$$R_4 = 5.6/3 K\Omega = R_1 \parallel R_2 \parallel R_3$$

$$R_4 = 1.8K\Omega$$

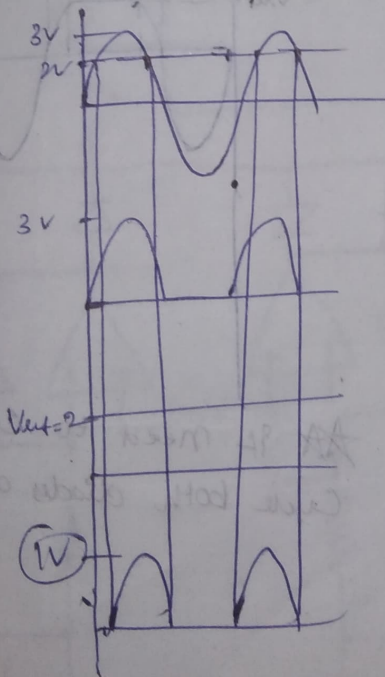

### (3) precision clipper:-

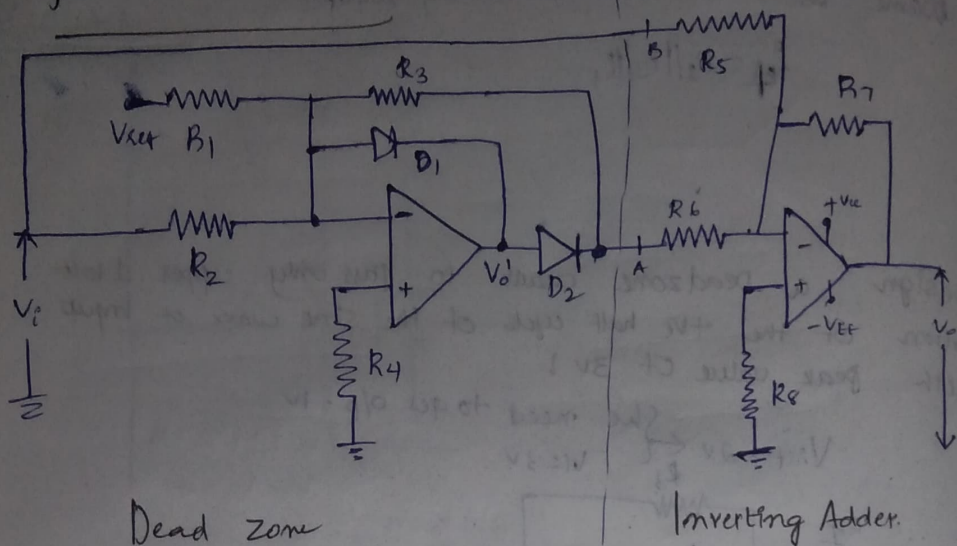

Dead zone

Inverting Adder.

(1) if  $V_i = +ve$        $V_{ref} = +ve$

$$V_{o1} = -ve$$

$D_2 = RB$

$D_1 = FB$

$$V_A = 0V \quad ; \quad V_B = V_i$$

{ No amplification since  $R_5 = R_6 = R_7 = R_8$  }

$$V_o = -(V_A + V_B)$$

$$V_o = -V_i$$

(2) if  $V_i = -ve$ ,  $V_{ref} = +ve$

$$V_{o1} = +ve \quad \{ \text{if } V_i > V_{ref} \}$$

$D_1 = RB$

$D_2 = FB$


$$V_A = -(V_i + V_{ref}) = -(-V_i + V_{ref}) = V_i - V_{ref}$$

$$V_B = -V_i$$

$$V_o = -(V_A + V_B)$$

$$= -[V_i - V_{ref} + V_i]$$

$$V_o = V_{ref}$$

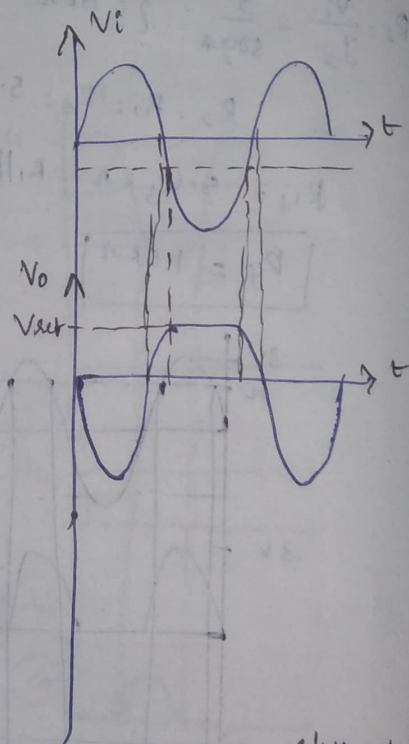


★ if need to clip at negative cycle both diodes are reversed.

clip - off some part in both triage -ve cycles:-


CLAMPERS

(1) DIODE CLAMPING CKT

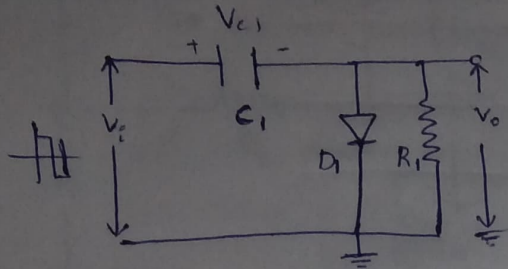

1)  $V_i = +ve$ ,  $D_1$ : fB {short ckt}  
 $C_1$  charging  $V_{C1} = V_i - V_F$   
 $V_o = V_i$

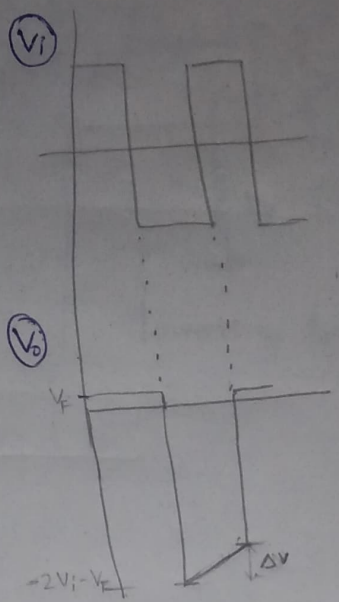2)  $V_i = -ve$ ;  $D_1$ : RB {open ckt}  
 $C_1$ : Discharging through  $R_1$   
 $V_o = V_i - V_{C1}$   
 $= -V_i - (V_i - V_F)$   
 $= -2V_i + V_F$




Because of " $R_1$ " capacitor discharging there is a limit

Drawback:


Due to " $V_F$ "  $V_o = -2V_i + V_F$  which not equal to  $-2V_i$   
 So, we use op-amp ~~for~~ clamping.

(2) Precision Clamping circuit:-

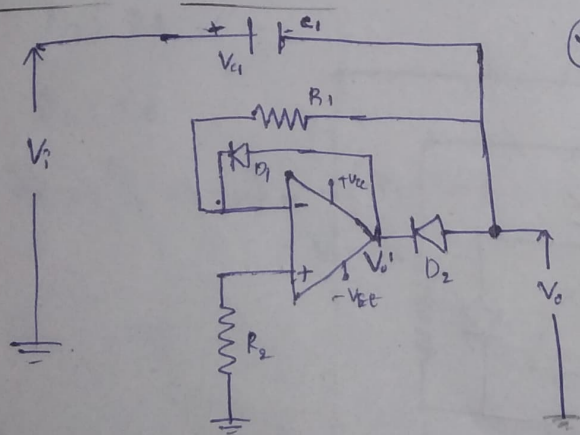

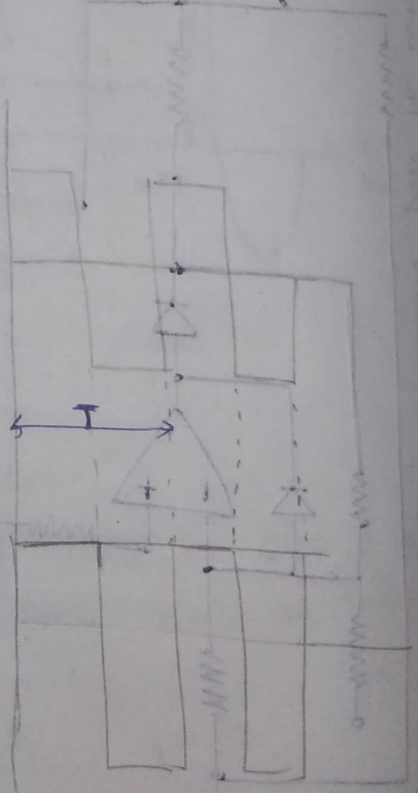1)  $V_i \ge +ve$ ;  $V_o = -ve$   
 $D_2$ : fB;  $D_1$ : RB  
 Due to closed path  
 Capacitor starts charging towards  $V_{c1}$

$V_{C1} = V_i$   
 $V_o = V_i - V_{C1} = 0$



The i/p of inverting terminal is same as the i/p of non-inverting terminal.

Since non-inverting terminal is grounded i/p of inverting terminal is zero.

$$V_i = -V_e ; V_o' = +V_e$$

$$D_1 = FB \quad D_2 = RB$$

$$V_o = V_i - V_{i_1}$$

$$= -V_i - V_i$$

$V_{i_1} = V_i$  } During charging

$$V_o = -2V_i$$

Design:-

$$1) C_1 R_s = T/2 \quad \{ R_s: \text{source resistance} \}$$

$$C_1 = \frac{T}{2R_s}$$

$$C_1 = \frac{1}{2fR_s}$$

$$2) I = \frac{2V_i}{R_1} \quad \{ 2V_i: \text{Max}^m \text{ o/p} \}$$

$$3) C = \frac{Q}{V} = \frac{IT}{V}$$

$$C_1 = \frac{I}{\Delta V} T/2$$

$$C_1 = \frac{[2V_i/R_1] T}{\Delta V} \frac{1}{2}$$

$$C_1 = \frac{V_i T}{R_1 \Delta V}$$

$$C_1 = \frac{V_i}{f R_1 \Delta V}$$

$$R_1 = \frac{V_i}{f C_1 \Delta V}$$

$$4) R_2 = R_1$$

(1) A  $\pm 5V$ ,  $10KHz$  square wave from a signal source with a resistance of  $100\Omega$  is to have its positive peak clamped precisely at ground level. Tilt on the output should not exceed 1% of the peak amplitude of the wave? Design a suitable op-amp precision clamping circuit with the power supply of  $\pm 12V$ ?

$\pm 5V \Rightarrow V_i$        $f = 10kHz$        $100\Omega = R_s$

$V_o = (2V_i) = 10V$

$C_1 = \frac{1}{2fR_s} = \frac{1}{2 \times 10^4}$

$C_1 = 0.5\mu F$

$I = 2V_i / R_1 = 10 / R_1$

$\Delta V = 17.0f5V$


$R_1 = \frac{V_i}{f C_1 \Delta V}$

$\Delta V = 0.05$

$= \frac{5}{(10^4)(0.5 \times 10^{-6})(0.05)}$

$R_1 = 20K\Omega$

$R_1 = 18.18K\Omega$

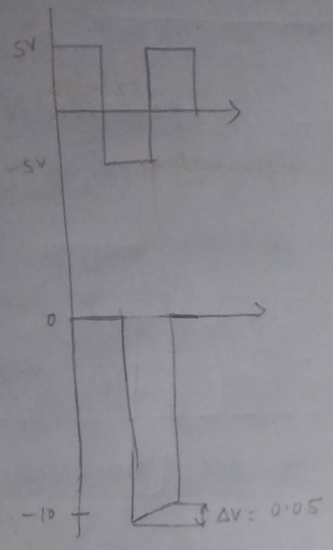

$C_1 = \frac{1}{2fR_s}$

$\frac{10V}{V} = 2$

$C_1 = \frac{1}{2fR_s}$

$C_1 = \frac{1}{2 \times 10^4}$

$C_1 = \frac{1}{20000}$



$R_1 = \frac{V_i}{f C_1 \Delta V}$

The word Design or synthesis of op-amp buffer circuit with the power supply of  $\pm 5V$ .  
 The input signal is a square wave with a peak-to-peak amplitude of 10V. The output signal is a square wave with a peak-to-peak amplitude of 50.0mV. The input signal is inverted and the output signal is not inverted. The gain of the circuit is 0.05. The circuit is a voltage follower.

# Peak Detectors:-

{ first Diode then capacitor }

## 1) Peak detector using diode:-

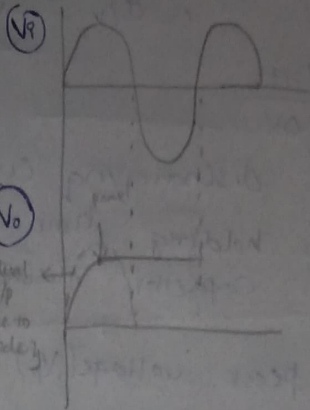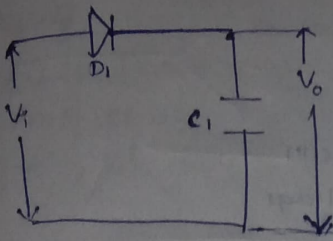

- 1)  $V_i = +ve$   
 $D_1$ : FB { closed loop }  
 $C_1$ : charging


due to diode  
 $V_i \neq V_{C_1}$  { not exactly equal to  $V_i$  }

- 2)  $V_i = -ve$   
 $D_1$ : Reverse Biased

12/3/20

## 2) Precision rectifier peak detector:-


{ non-saturated inverting }

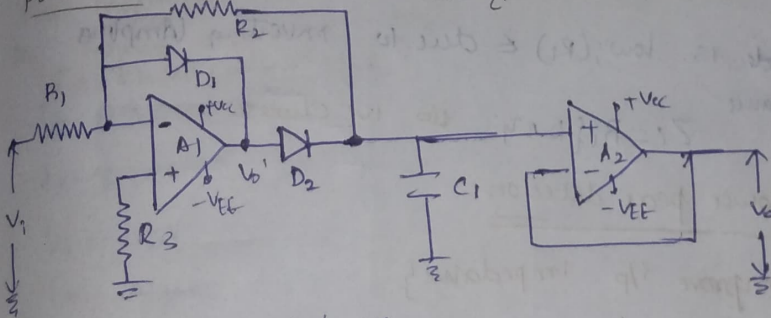

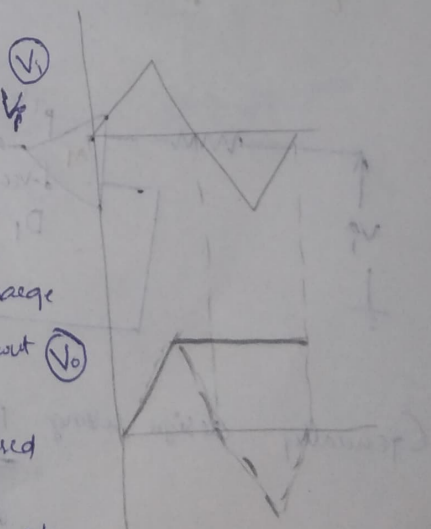- 1)  $V_i = +ve$ ;  $V_o = -ve$   
 $D_1$ : FB;  $D_2$ : RB  
 $C_1$  charges through  $R_1$  &  $R_2$  to peak  $V_i$
- 2)  $V_i = -ve$ ;  $V_o = +ve$   
 $D_1$ : RB;  $D_2$ : FB

since  $C_1$  has no path to discharge  
 capacitor holds same value throughout  $V_o$

Design:- A voltage follower is used  
 to isolate the capacitor  
 from discharging effect of  
 any load resistor





design:

We know that

$$Q = CV$$

$$C = Q/V = \frac{I \cdot t}{V}$$

$$C_1 = \frac{I_d t_h}{\Delta V}$$

$I_d$ : discharging current

$t_h$ : holding time of capacitor

$\Delta V$ : capacitor discharge voltage

For peak voltage ( $V_p$ ) & minimum sig rise time ( $t_r$ )

$$C_1 = \frac{I_{omax} \cdot t_r}{V_p}$$

$$I_{omax} = \frac{C_1 V_p}{t_r}$$

Minimum Slew rate is given by

$$S_{min} = 3 \frac{V_p}{t_r}$$


Drawback:

i/p impedance is low; ( $R_i$ ) & due to inverting Amplifier Impedance

$Z_i = R_i$  {key} so we choose

3) Voltage follower peak detector:-

{to improve i/p impedance}

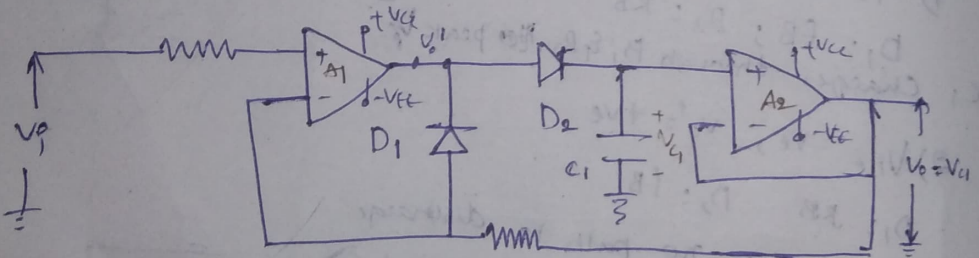

Generally design using BIFET


It have min<sup>m</sup>  
Capacitor leakage current

1) If  $V_i = +ve$ ,  $V_o = +ve$   
 $D_1: RB$   $D_2: FB$

\* Charging of  $C_1$  to  $V_p$ , b/w time  $A_2$   
 $V_i > V_o$  holds same value  
 $V_o = -ve$  {  $V_i < V_{c1}$  }  
 $D_1: FB, D_2: RB$  holds same voltage

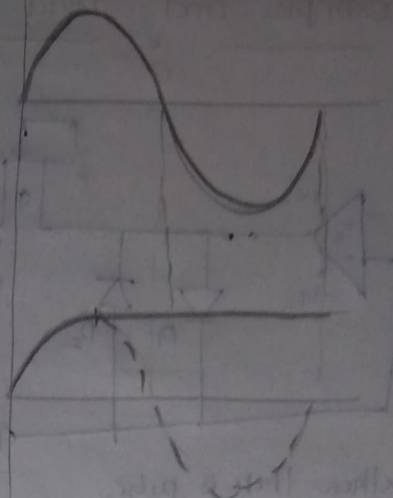2)  $V_i = -ve$ ,  $V_o = -ve$ ,  $D_2: RB, D_1: FB$

voltage pulse  
 $V_o - V_{c1}$   
 feedback  
 $A_1$



design:

\* same as precision peak detector

① Design voltage follower peak detector with pulse type signal voltage which has a peak value approximately 2.5V with rise time of 5μsec and the o/p voltage to be held at 2.5V for a time of 100μsec. the maximum o/p error is to be approximated 1%. calculate the required component values and specify o/p current, slew rate!

①  $V_i = 2.5V$

$t_r = 5\mu sec$

$V_o = 2.5V$

$t_h = 100\mu sec$

$\Delta V = 1\% \text{ of } V_p = 0.025$


$C_1 = \frac{I_d t_h}{\Delta V} = \frac{(1\mu A)(100\mu sec)}{0.025} = 4000 \text{ PF}$

$I_{o(max)} = \frac{C_1 V_p}{t_{r1}} = \frac{(4000PF)(2.5)}{(5\mu)} = 2 \text{ mA}$

$Slew\ rate = 3 \frac{V_p}{t_r}$   
 $= \frac{(3)(2.5)}{5\mu sec} = 1.5V/\mu sec$

Choose  $R_1 = R_2 = 1M\Omega$   
 { ckt designed using BIFETs }

# (\*) Sample and Hold Circuit:

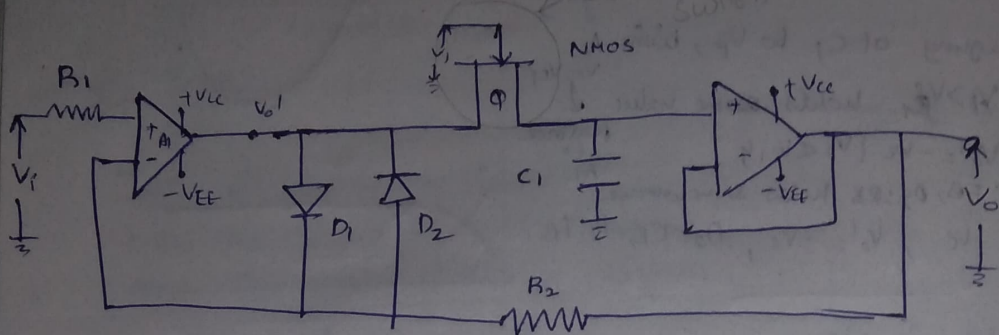

When there is pulse

$\Phi = \text{ON}$

When NO pulse

$\Phi = \text{OFF}$

1)  $V_i = +ve; V_{01} = +ve$

$D_1 = \text{FB}, D_2 = \text{RB}$

$\Phi = \text{ON}; C_1: \text{Charge to } V_i$

$\Phi = \text{OFF}; C_1: \text{No charging}$

2)  $V_i = -ve, V_{01} = -ve$

$D_1 = \text{RB}, D_2 = \text{FB}$

$\Phi = \text{ON}, C_1: \text{Discharging to } D_2$

